

Final Project: Configurable Logic Block

Team : Siddhant Mathur and Ruturaj A. Nanoti

1 DESIGN OF 2:1 MUX

1.1 Circuit Schematic

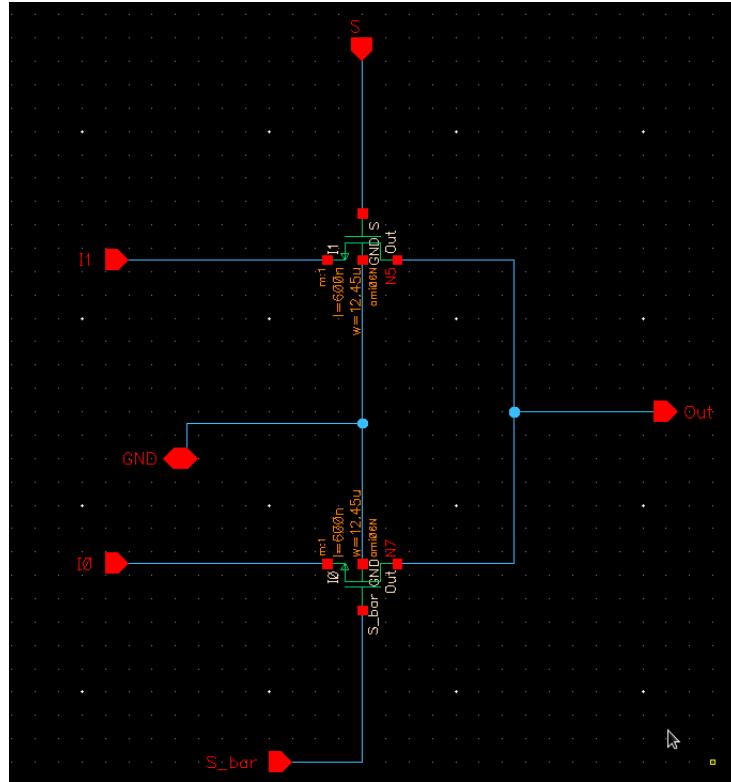


Figure 1: Mux 2:1 - Circuit Schematic

We have used pass transistor logic for our 2:1 Mux design because it uses lesser inverters compared to transmission logic. We have removed the inverter from the select line of the 2:1 Mux and have made it common for the select lines for each of the 4 stages in our 16:1 Mux so that we can cut down on the number of transistors in our 16:11 Mux. This makes our base design relatively more optimized in terms of area compared to having an inverter in each of the 2:1 Mux's.

The optimized sizings we used for the LUT were (we have explained how we arrived at those values in the later sections):

Width of PMOS: 13.5 μm

Width of NMOS: 12.5 μm

These sizings were obtained using a combination of our *Elmore Delay* model for the LUT and the *parametric analysis* performed on Cadence to assist us in reaching the optimal size. The circuit was optimized for delay , while keeping in mind the area that the LUT will contribute to the design of our Configurable Logic Block. Fig. 1 shows the circuit schematic for the 2:1 Mux, which forms a basic block in the design of our LUT.

1.2 Symbol For 2:1 Mux

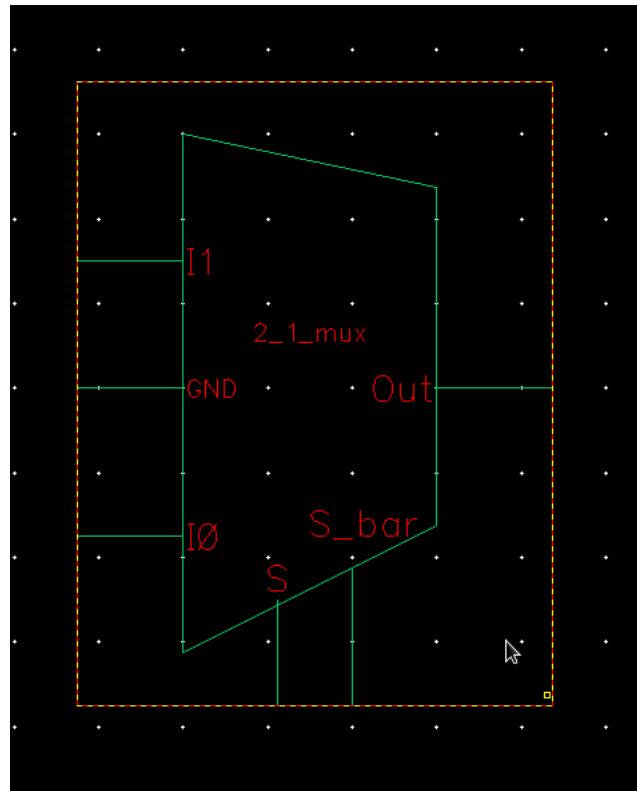


Figure 2: Mux 2:1 - Symbol

1.3 Test Schematic Using Symbol

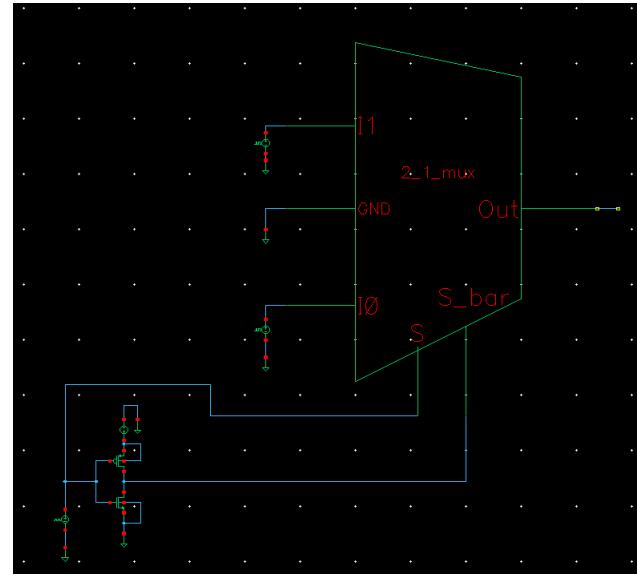


Figure 3: Verification using the symbol

Fig. 3 shows the test schematic that was setup to verify the functionality of our 2:1 Mux. For testing our design, we have cycled through the *address bit* which will make the output follow the input based on the state of the address bit. The inputs are being fed by two different *vpulse* sources, where one has a period that is double the other, that allows us to test the possible cases.

1.4 Functionality Verification of 2:1 Mux

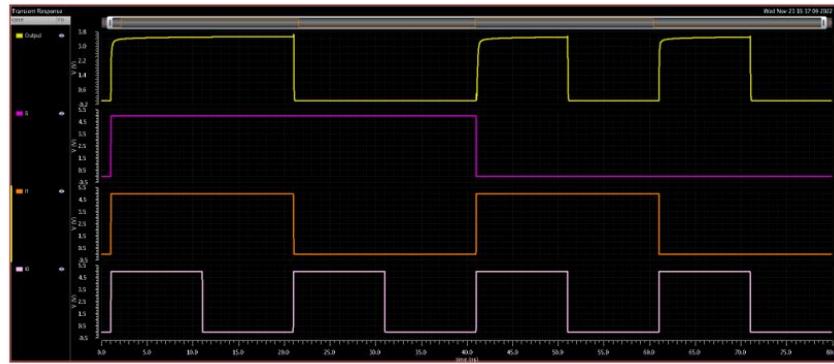


Figure 4: Verification Graph using the symbol

This waveform proves that the 2:1 Mux functions accurately. According to the design of our 2:1 Mux, the output should follow I1 when S=1 and I0 when S=0. This is exactly what is replicated in the above waveforms which confirms the functionality of our 2:1 Mux.

2 16:1 MUX DESIGN USING 2:1 MUX

In the 16:1 Mux design , we have used an inverter for the select lines for each of the 4 stages. This was done to avoid having an inverter in each of the 2:1 Mux's as they would have been redundant in the 16:1 Mux design.

The optimized sizings we considered were (explained in the later sections):

Width of PMOS: 13.5 μ m

Width of NMOS: 12.5 μ m

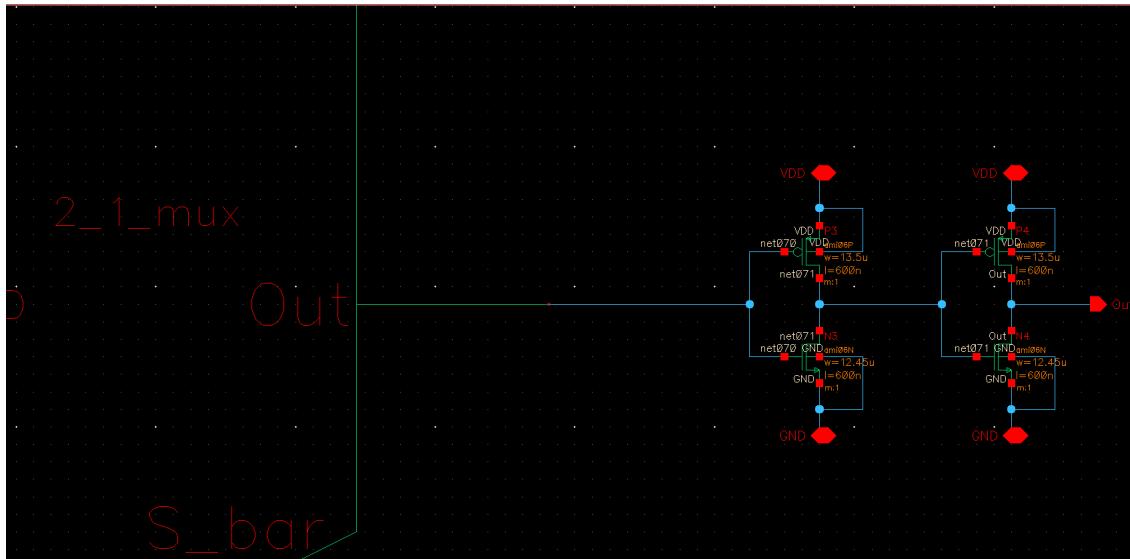


Figure 5: Zoomed in view of the 16:1 Mux

Fig.5 denotes the sizings we have used for the 16:1 Mux as mentioned above. Here , we can see that the sizings have also been maintained for the restoration buffer after the last stage of our 16:1 Mux .This ensures rail to rail output since, the pass transistors cause a V_T drop.

2.1 Circuit Schematic

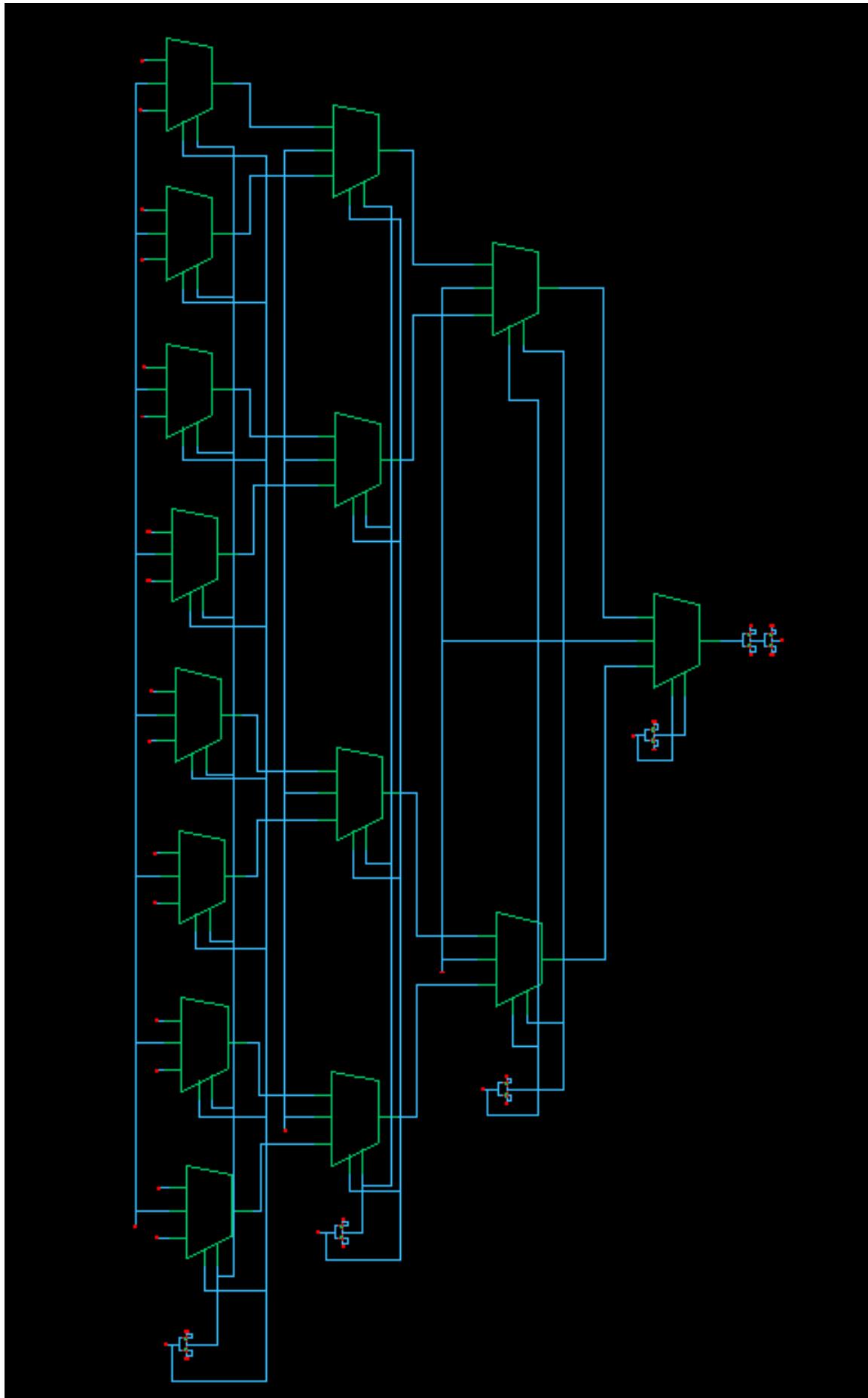


Figure 6: Circuit Schematic - 16:1 Mux

2.2 Symbol for the 16:1 Mux

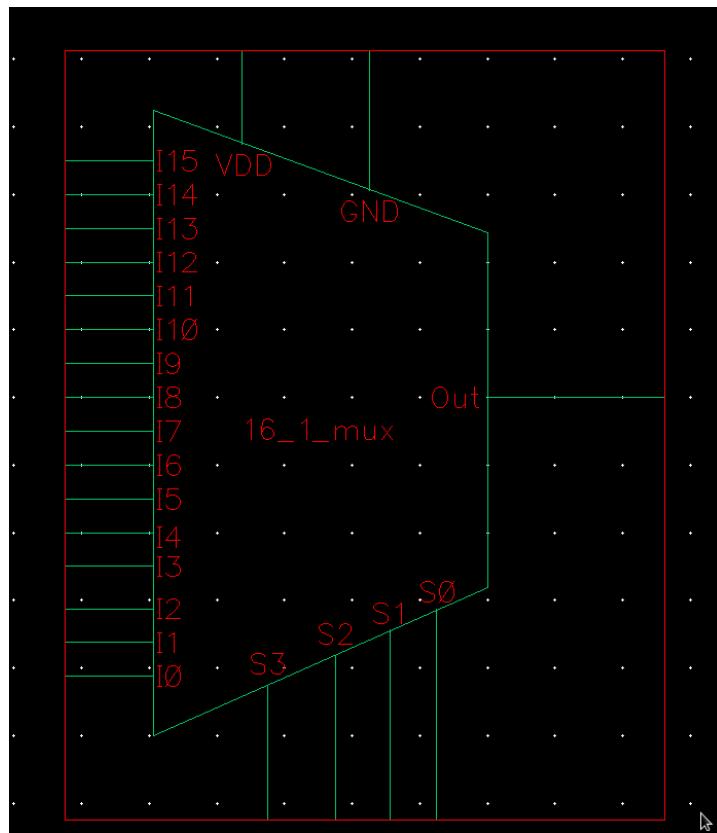


Figure 7: Symbol - 16:1 Mux

2.3 Test Schematic Using Symbol

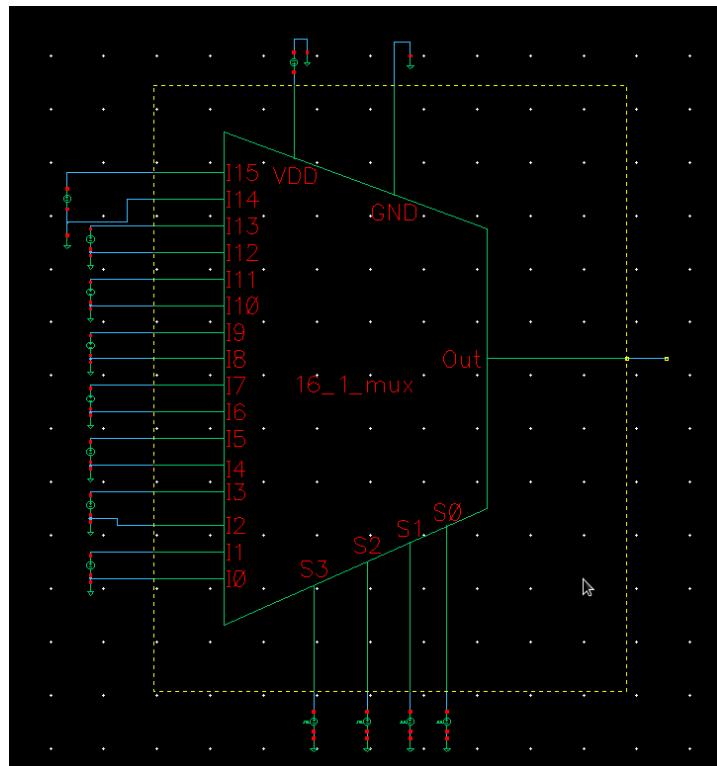


Figure 8: Test Schematic - Symbol 16:1 Mux

Fig. 8 shows the test schematic that we setup to verify the functionality of our 16:1 Mux design. For this, we have connected the alternate bits from I_{15} to I_0 to a 5V supply. This enables us to test switching input cases and verify if our design conforms to all possible input cases.

2.4 Functionality Verification of 16:1 Mux



Figure 9: Functionality Verification Graph

As can be seen in the verification plot (Fig. 9), the inputs are alternating between 1 and 0 and the address bits are being cycled through with different pulse widths and periods to test for all possible 16 cases. Thus, the output follows all the bits at the input and verifies the working of our 16:1 Mux.

2.5 Maximum Worst Case Delay

We measure the delay between the S_3 select line and the output before the load. The S_3 select line (for the leftmost stage) is our LSB and the S_0 select line (for the rightmost stage) is our MSB. We have identified the case that contributes to the maximum worst case delay as when S_3 is switching and the other 3 select lines are kept at a logical high (VDD).

This would mean that the output keeps toggling between In_{14} and In_{15} since the select lines would either be 1110(In_{14}) or 1111(In_{15}).

We have switched S_3 since this select line is driving the most number of 2:1 MUXs and would result in higher parasitic capacitance as compared to the other 3 stages. Thus, it makes sense to switch the select line(S_3) that has to drive the highest load and is associated with the highest capacitance. The inputs to all the select lines are given through inverters and the out pin of the 2:1 Mux is connected to In_{15} of the 16:1 Mux.

2.6 Parametric Sweep Graph

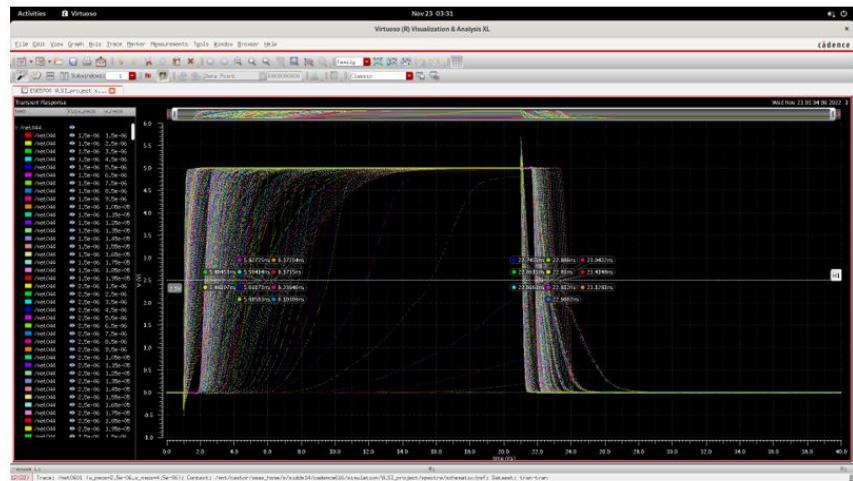


Figure 10: Overall Parametric Sweep

2.7 Delay Using Parametric Sweep



Figure 11: Delay using chosen sizing from Parametric Sweep

For the PLH and PHL values,

$$\tau_{PLH} = 2.3561ns - 1.20239ns = 1.15371ns$$

$$\tau_{PHL} = 21.9131ns - 21.1371ns = 0.776ns$$

So, the worst-case delay comes out to be **1.15371 ns**.

The optimized sizings we considered were:

Width of PMOS: 13.5 μm

Width of NMOS: 12.5 μm

The sizing for the inverter that drives the our 16:1 mux for the worst delay case, the transistors for 2:1 mux and the buffer used for restoration at the end before the load are as mentioned above. The inverters driving the select lines of our DUT need to have the same drive strength as a 2:1 mux; the buffer used for restoration also needs to be sized the same since it is being driven by a single 2:1 mux.

The transistors in the inverters of the load are sized as to act as a $100C_g$ load.

Width of the PMOS in the inverter of the load: 75 μm

Width of the NMOS in the inverter of the load: 75 μm

We could have reduced the worst-case delay further by increasing the sizes of the PMOS and NMOS even more, however, we did not prefer increasing the sizes beyond a point as that would lead to an increase in the total area. Thus, we settled at the above mentioned sizings for our design.

3 SRAM CELL

3.1 Circuit Schematic

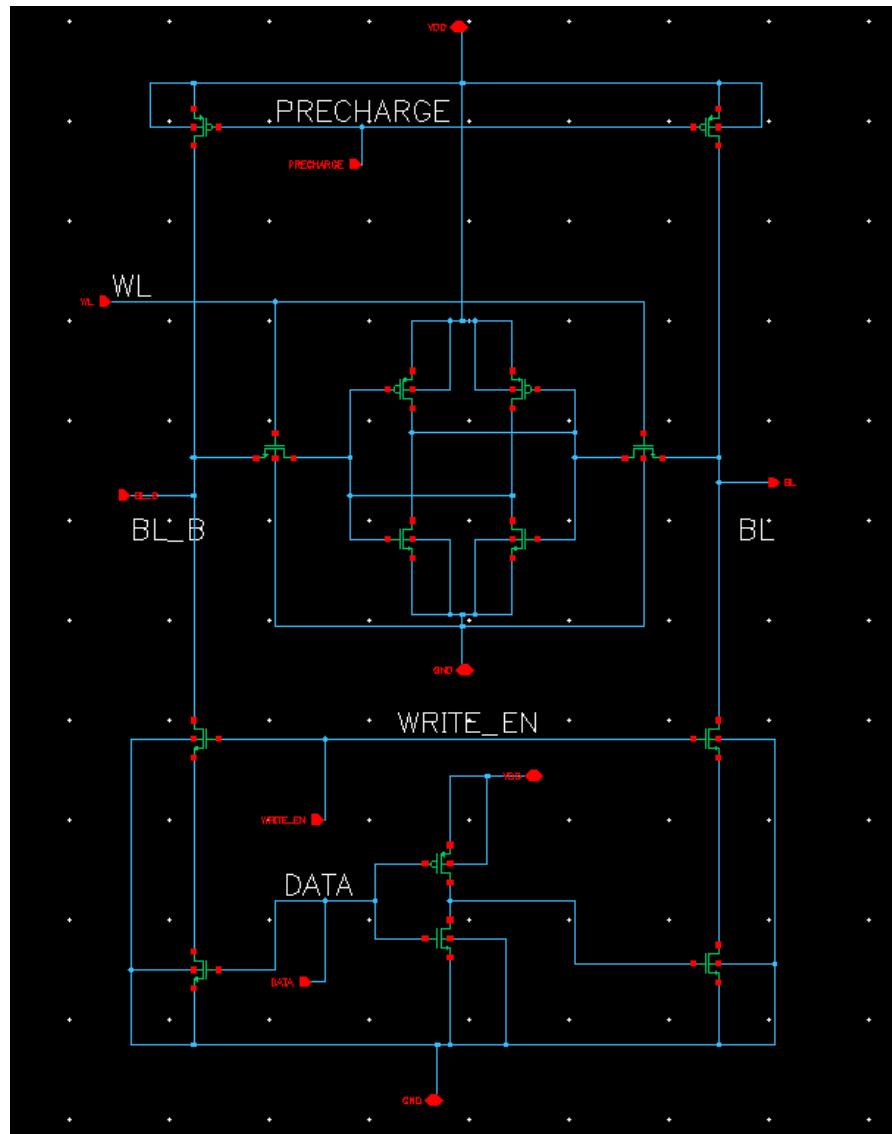


Figure 12: 6-T SRAM Cell

We have designed a 6-T SRAM cell which stores data in cross-coupled inverters and is used in most commercial chips.

3.2 Proof of sizings

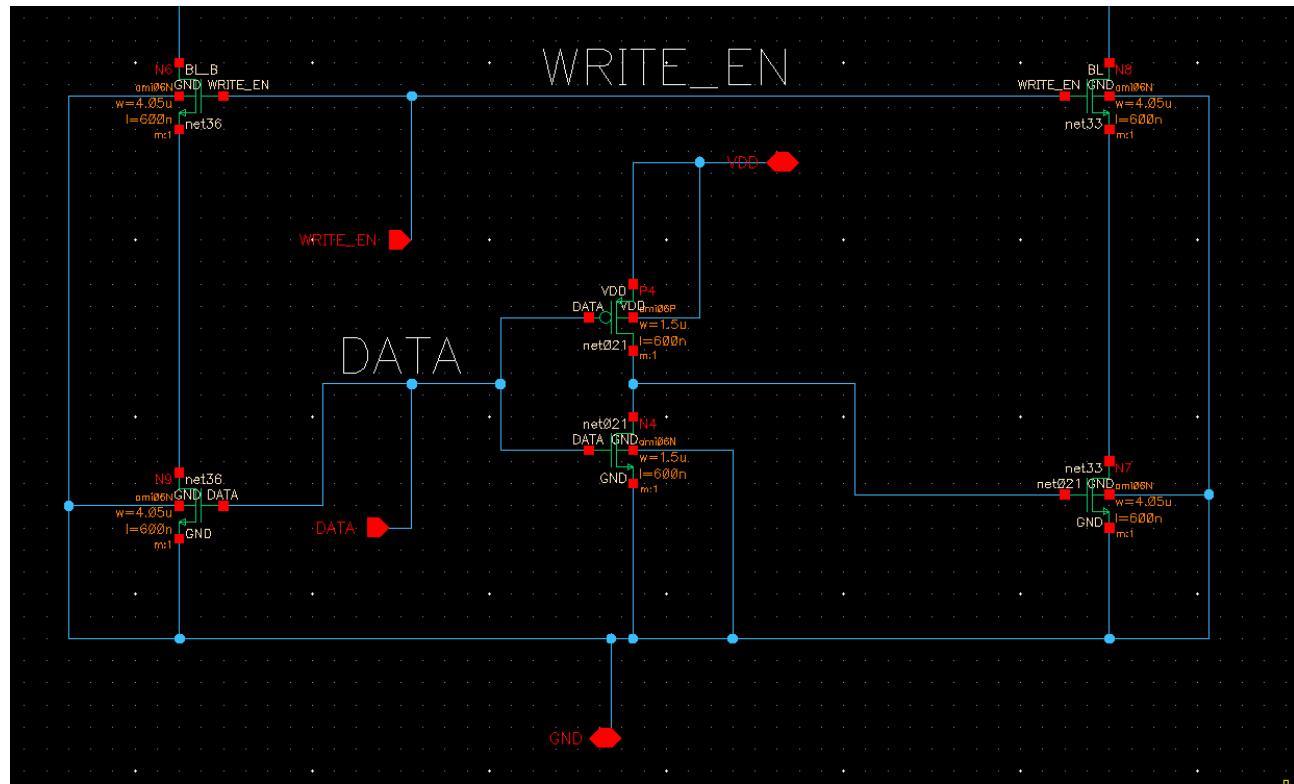


Figure 13: Zoomed in View of the SRAM Cell - 1

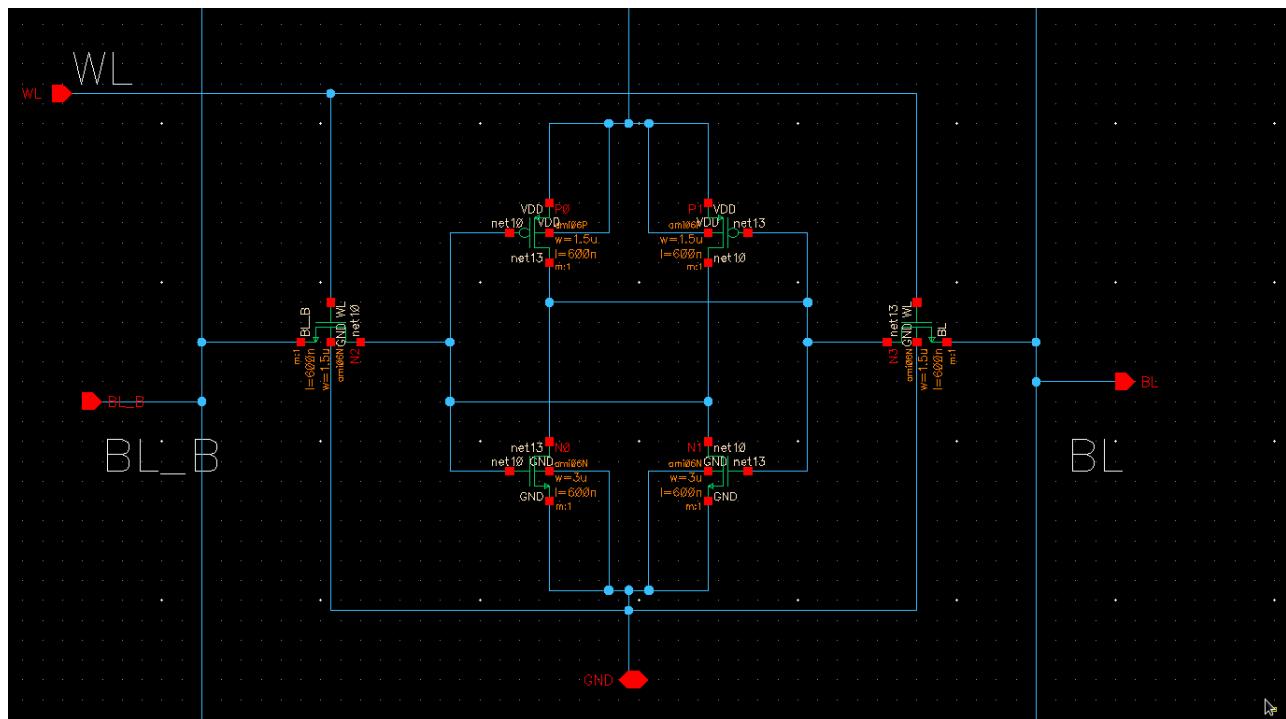


Figure 14: Zoomed in View of the SRAM Cell - 2

3.3 Sizings used for the SRAM cell

We have designed a traditional 6-T SRAM cell and set the size of the NMOS' in the cross coupled inverters to $3\mu\text{m}$.

Shown below is a representation of the 6-T SRAM :

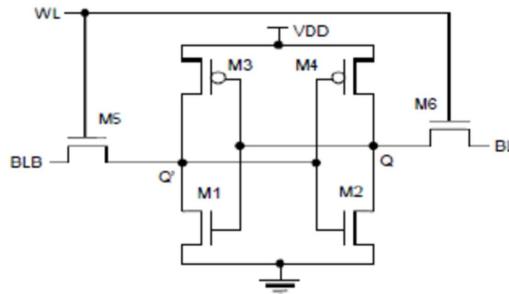


Figure 15: 6T - SRAM Cell

We have set the sizes of the NMOS M_1 and M_2 as $3\mu\text{m}$ because it is important for the NMOS M_1 to be stronger than M_5 as during discharging , the bitline bar discharges through M_5 and M_1 . Thus, we have sized the M_1 NMOS to be greater than NMOS M_5 . The same applies to the NMOS' M_2 and M_6 where $M_2 \gg M_6$ for the above mentioned reason. This is done to ensure read stability.

The reason why we did not increase the sizes of the NMOS' of the cross coupled inverter beyond $3\mu\text{m}$ is that all bit cells of a single SRAM cell should ideally be small to make sure that the memory cell does not end up becoming too bulky. The NMOS' in the write circuitry are set to $4\mu\text{m}$ to ensure write stability. These sizings were not arrived at through parametric analysis but through ratios suggested for the general functionality of a 6-T SRAM cell.

3.4 Symbol



Figure 16: 6T - SRAM Cell Symbol

3.5 Testing of a single SRAM cell

The SRAM cell is tested with a pattern that makes sure the data stored in the cell does not get corrupted when performing a read. This is tested when storing both '1' and '0'. A write is performed by driving the data onto the bitline and then raising the word line, and then a read operation is performed twice to make sure that the read doesn't corrupt the data.

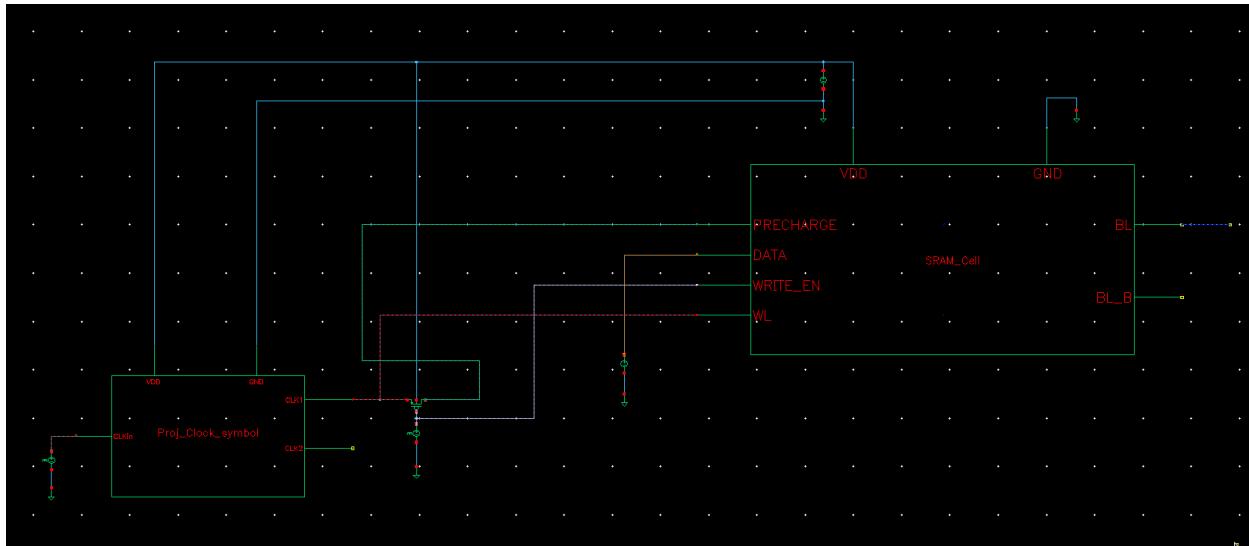


Figure 17: 6T - SRAM Cell Circuit Schematic : Testing with storing "1"

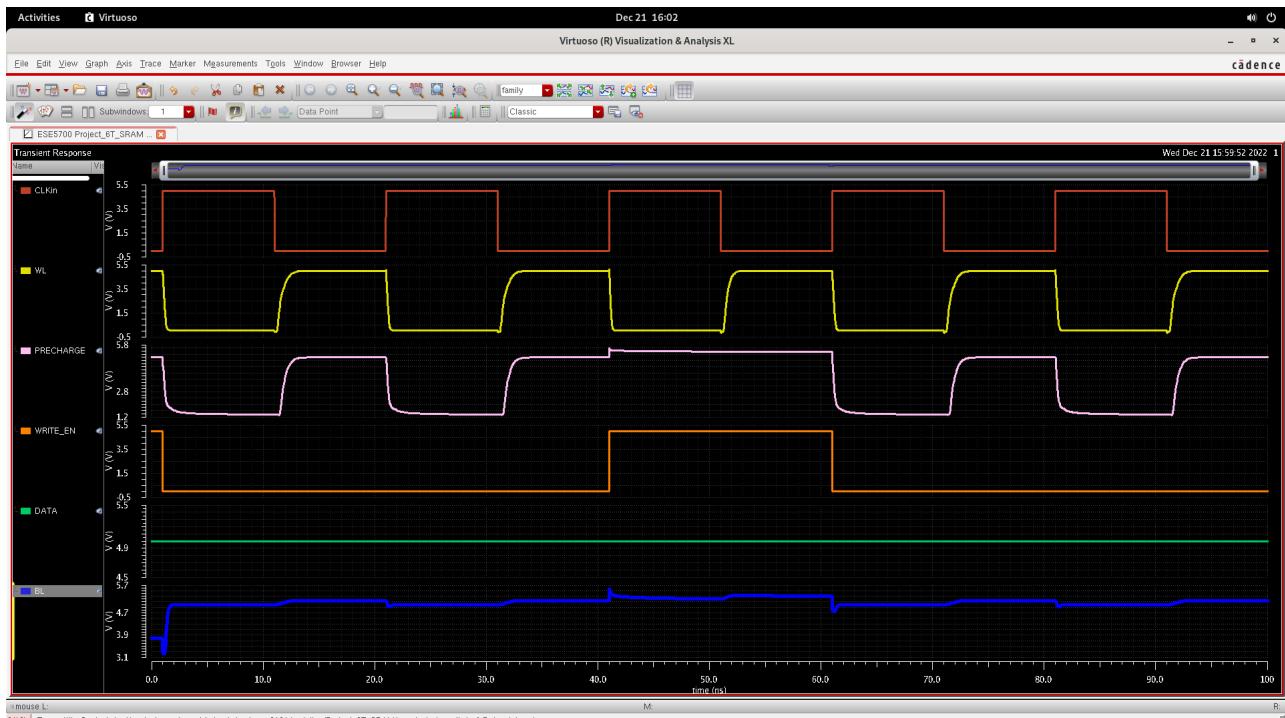


Figure 18: Verification Graph - 1

Fig. 17 and 18 depict that our SRAM is functioning just as expected. In this, we performed a read operation twice (for testing the nature of the read operation - destructive or non-destructive) and then wrote a 1 into the cell by driving the data onto the bitline, and then raising the word line. Upon writing a 1 into the cell , we then perform the read operation twice to make sure that our read is non-destructive, i.e. the data stored in the SRAM cell is not corrupted. The BL waveform shows that the SRAM is working properly.

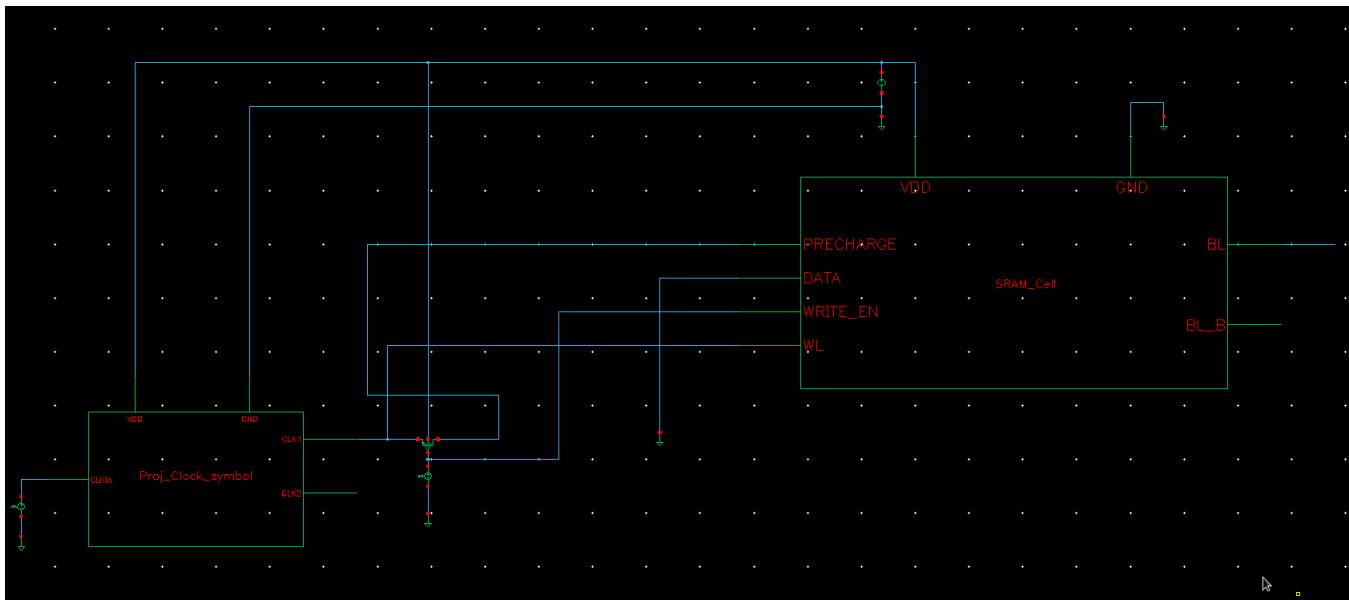


Figure 19: 6T - SRAM Cell Circuit Schematic : Testing with storing "0"

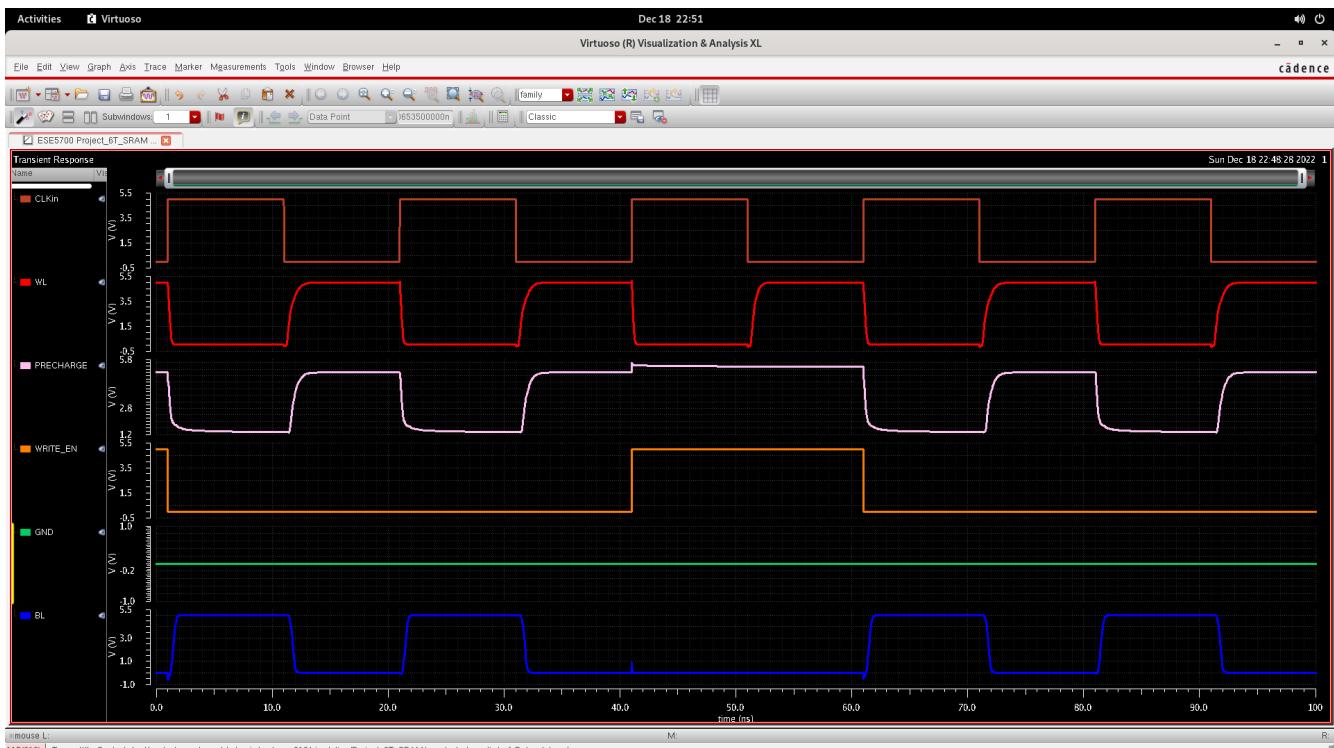


Figure 20: Verification Graph - 2

Fig. 19 and 20 depict that our SRAM is functioning just as expected. In this, we performed a read operation twice (for testing the nature of the read operation - destructive or non-destructive) and then wrote a 0 into the cell by driving the data onto the bitline, and then raising the word line. Upon writing a 0 into the cell , we then perform the read operation twice to make sure that our read is non-destructive, i.e. the data stored in the SRAM cell is not corrupted. The BL waveform shows that the SRAM is working properly.

3.6 Layout

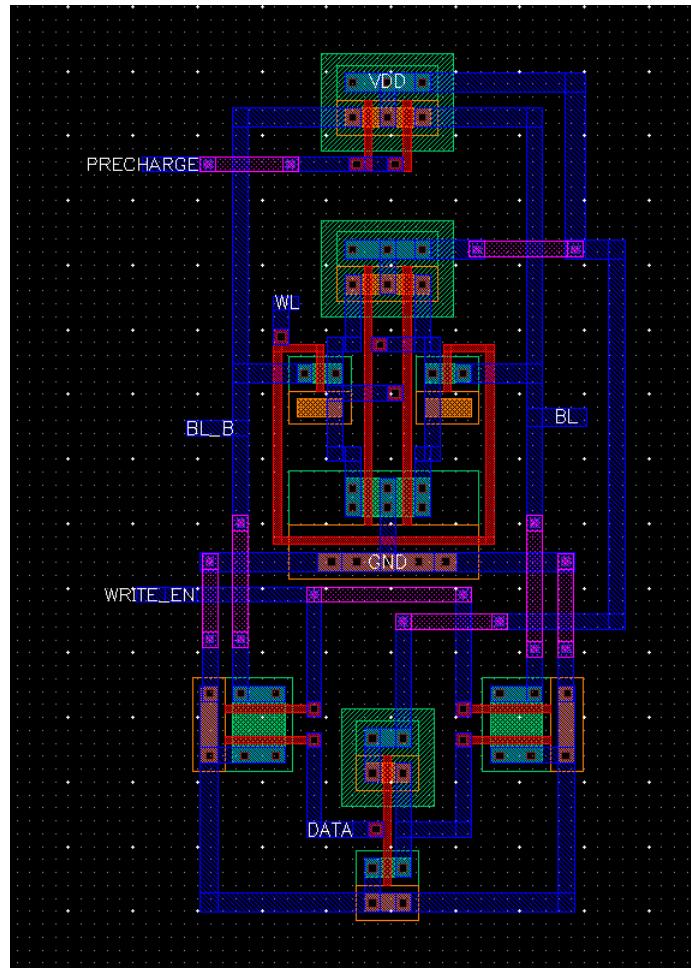


Figure 21: 6T - SRAM Cell Layout

3.7 Proof of Passing DRC

Figure 22: 6T - SRAM Cell DRC

3.8 Proof of Passing LVS

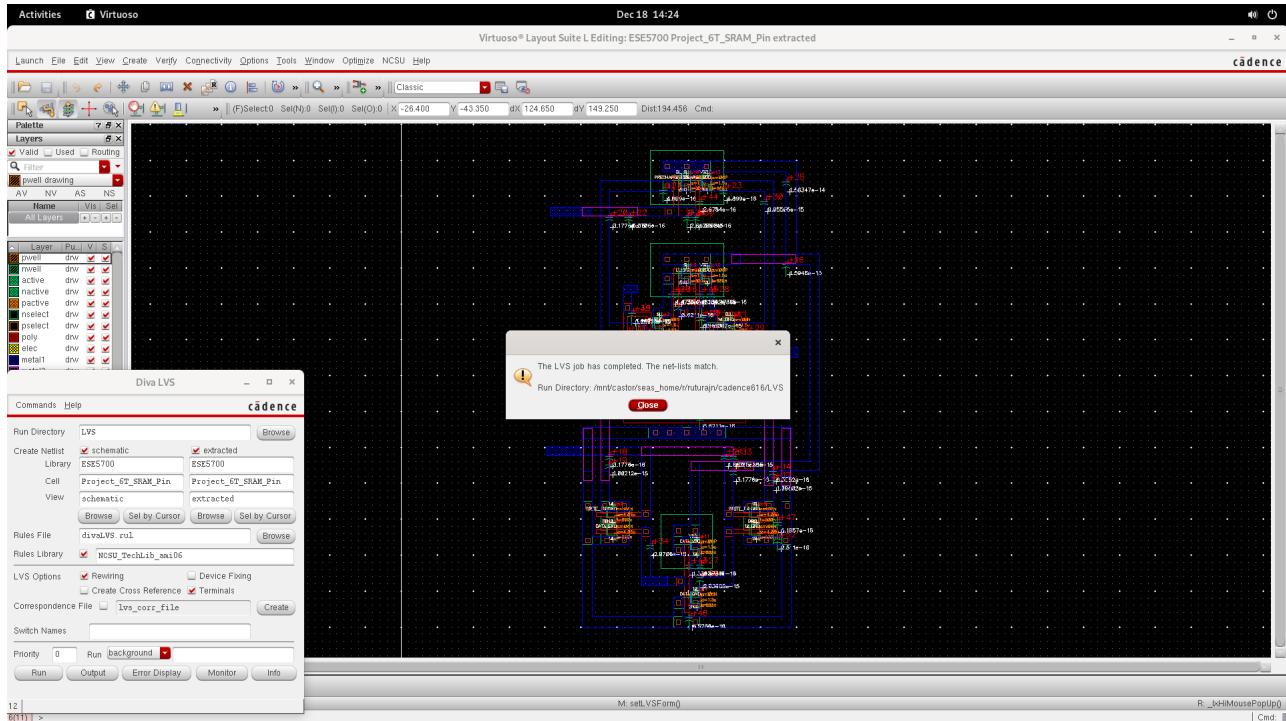


Figure 23: 6T - SRAM Cell LVS

```

Activities  @ Virtuoso          Dec 18 14:25
File Edit View Help
/mnt/castor/seas_home/r/ruturajn/cadence616/LVS/si.out
cadence

#DIV/6T-SRAM_LVS version 6.1.0.09/01/2015 15:36 (ejfnl105) #
Command line: /opt/pellicc/software/ic-design/cadence/ICE16/tools/lrv86/dfl1/bin/32bit/LVS -dir /mnt/castor/seas_home/r/ruturajn/cadence616/LVS -l -s -t /mnt/castor/seas_home/r/ruturajn/cadence616/LVS/layout /mnt/castor/seas_home/r/ruturajn/cadence616/LVS/schematic
Line watching is enabled.
Net swapping is enabled.
Using table correspondence points.
Compiling Diva LVS rules...
Net-list summary for /mnt/castor/seas_home/r/ruturajn/cadence616/LVS/layout/netlist
  count
  13   nets
  5   terminals
  5   pmos
  9   nmos

Net-list summary for /mnt/castor/seas_home/r/ruturajn/cadence616/LVS/schematic/netlist
  count
  13   nets
  5   terminals
  5   pmos
  9   nmos

Terminal correspondence points
N13  M1  EL
N12  M9  EL_B
N10  M8  DATA
N8   M11 GND
N7   M5  PRECHARGE
N4   M3  VDD
N9   M2  VSS
N11  M6  WRITE_EN

Devices in the netlist but not in the rules:
  scope netlist
Devices in the rules but not in the netlist:
  cap nfet pfet nmos4 pmos4

The net-lists match.
      layout  schematic
un-watched      0      0
  revised       0      0
size across     0      0
  pruned       0      0
  active       14     14
  total        14     14

      nets
un-watched      0      0
  merged       0      0
  pruned       0      0
  active       13    13
  total        13    13

      terminals
un-watched      0      0
  watched but different type  0      0
  total         8      8

Probe files from /mnt/castor/seas_home/r/ruturajn/cadence616/LVS/schematic
devbad.out:
netbad.out:
wrgenout.out:
termbad.out:
13 |
```

Figure 24: 6T - SRAM Cell LVS Output 1

```

Activities  Virtuoso  Dec 18 14:25
/mnt/castor/seas_home/r/ruturajn/cadence616/LVS/si.out  cadence
File Edit View Help

Terminal correspondence points
N1 M9 EL_B
N12 M8 DATA
N10 M1 GND
N5 M11 PRECHARGE
N7 M5 VDD
N14 M3 WL
N11 M6 WRITX_EN

Devices in the netlist but not in the rules:
probe.out:
Devices in the rules but not in the netlist:
cap nfet pmos4 pmos4

The net-lists match.

layout schematic instances
un-matched 0 0
resolved 0 0
size errors 0 0
pruned 0 0
active 14 14
total 14 14

nets
un-matched 0 0
merged 0 0
pruned 0 0
active 13 13
total 13 13

terminals
un-matched 0 0
matched but different type 0 0
total 8 8

Probe files from /mnt/castor/seas_home/r/ruturajn/cadence616/LVS/schematic
devbad.out:
netbad.out:
wergnet.out:
terbad.out:
prunenet.out:
prunedev.out:
audit.out:

Probe files from /mnt/castor/seas_home/r/ruturajn/cadence616/LVS/layout
devbad.out:
netbad.out:
wergnet.out:
terbad.out:
prunenet.out:
prunedev.out:
audit.out:
13

```

Figure 25: 6T - SRAM Cell LVS Output 2

4 CLOCK

This circuit provides us with two out of phase clocks (generated using a single clock) that are used to run our configurable logic block. The clock was designed using NOR gates and inverters. All transistors used to design the clock are minimum sized.

4.1 Schematic

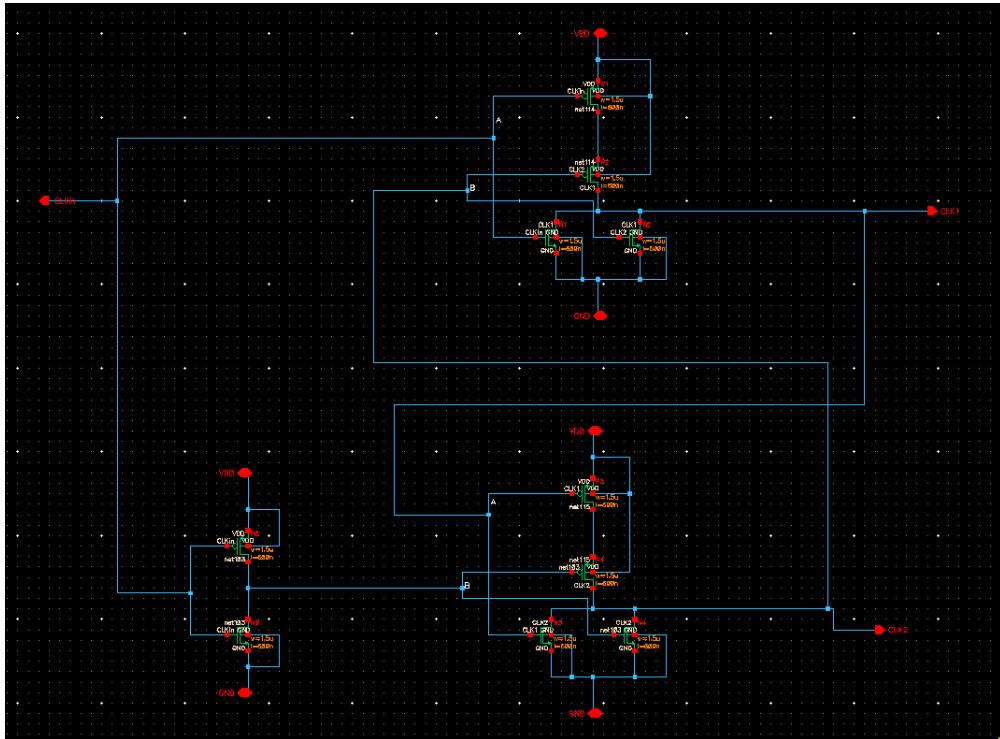


Figure 26: Circuit Schematic for Clock

4.2 Symbol

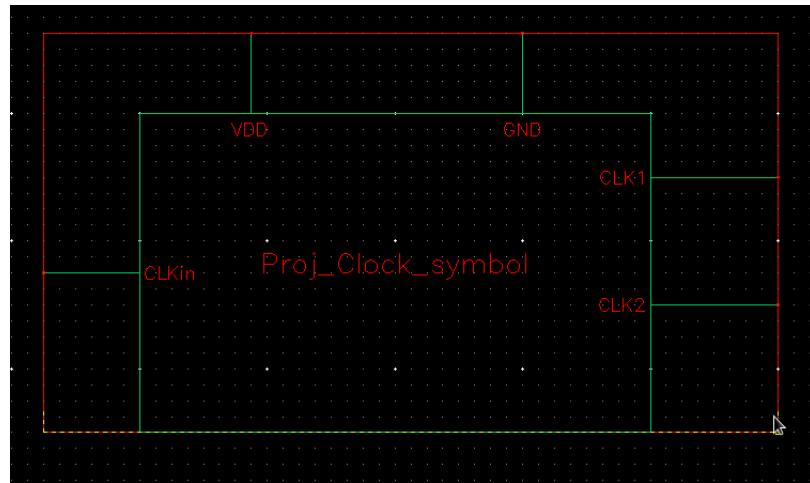


Figure 27: Circuit Schematic for Clock

4.3 Test schematic using symbol

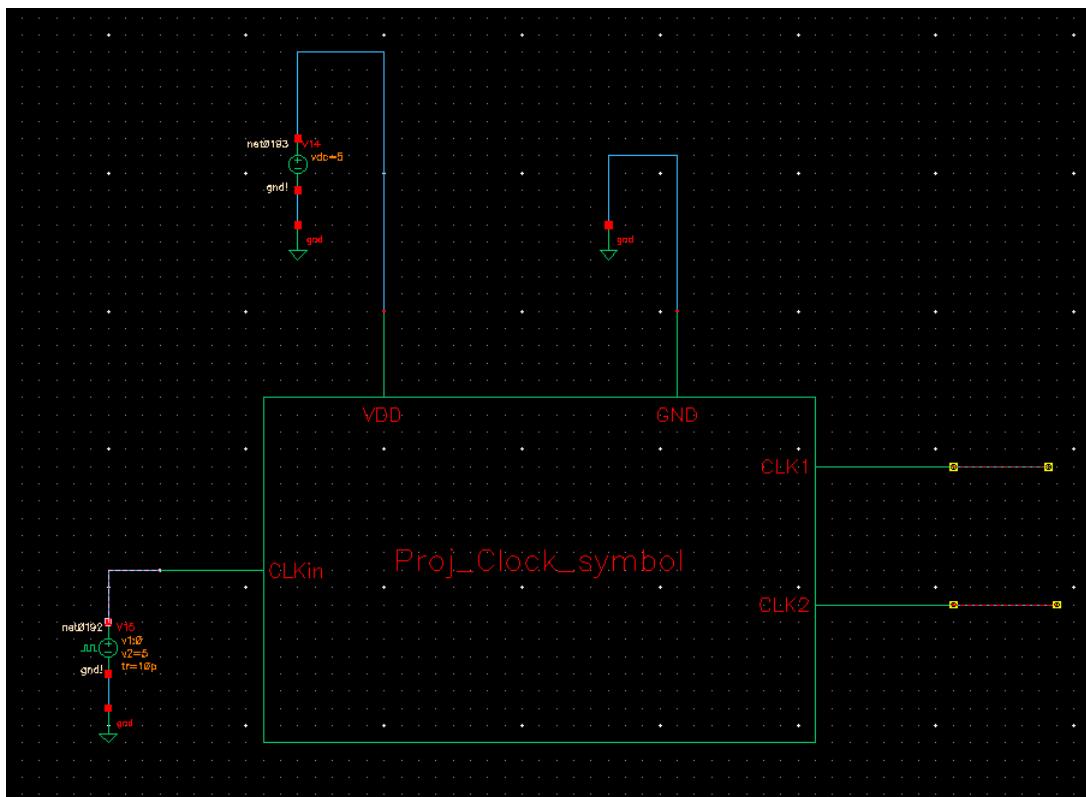


Figure 28: Test Schematic for Clock

4.4 Verification using Symbol

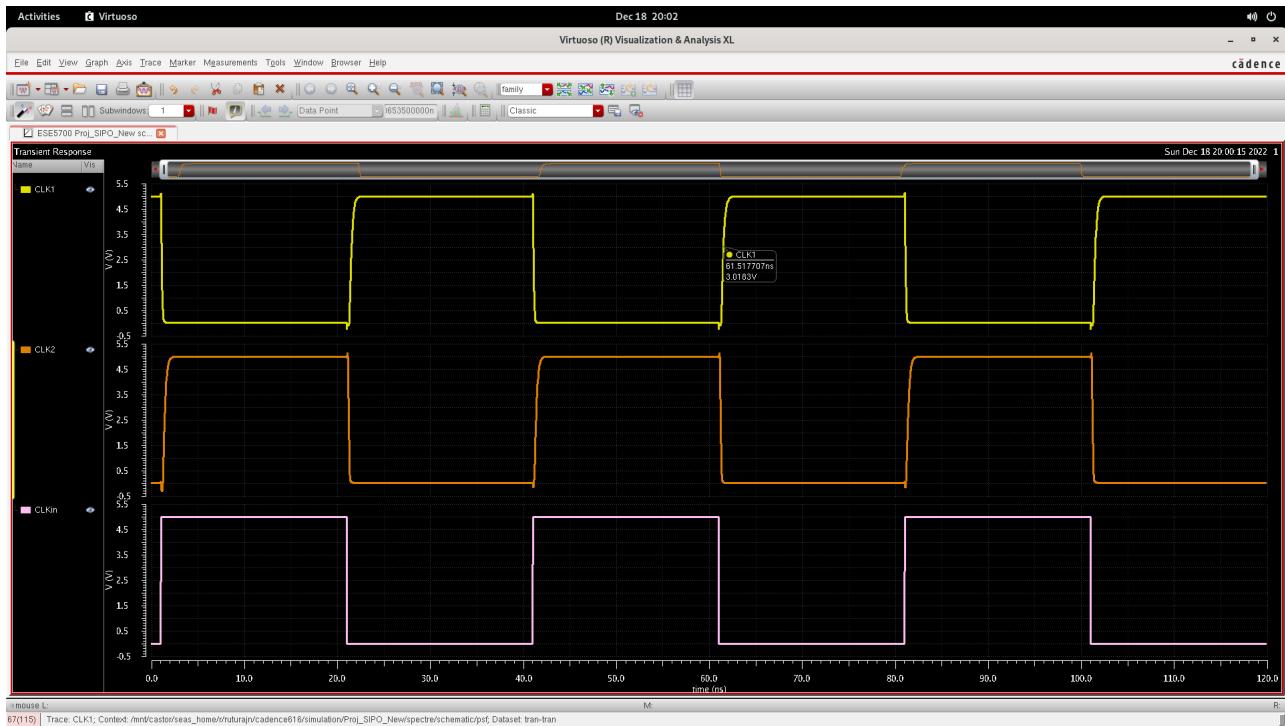


Figure 29: Verification Graph - Clock

From this plot , it is evident that we are able to generate two out of phases clocks using a single clock. Here CLK_2 follows our input CLK_{in} and CLK_1 is the opposite / out of phase.

4.5 Layout

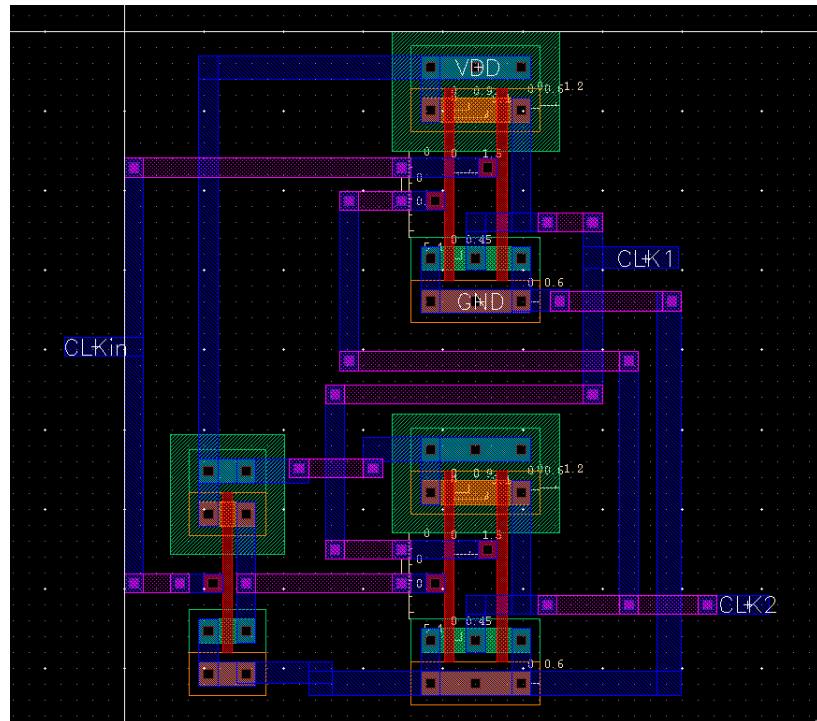


Figure 30: Layout - Clock

4.6 Proof of Passing DRC

```

Activities   Virtuoso  Dec 18 20:35
Virtuoso® 6.1.6 - Log:/mnt/castor/seas_home/r/ruturajn/CDS.log  cädence
File Tools Options Help

executing: drc(geomEdgEdge("elec") geomNetEdge("metal2") (sep < (lambda * 2.0)) errMsg)
executing: saveDerived(geomNetEdge(netsAll elec diffNet) errMsg)
executing: saveDerived(geomNetEdge(netsAll elec diffNet) (sep < (lambda * 2.0)) errMsg)
executing: saveDerived(geomNetEdge(netsAll elec diffNet) (width < (lambda * 2.0)) errMsg)
executing: drc(TransistorEleEdge (sep < (lambda * 3.0)) errMsg)
drc(TransistorEleEdge (width < (lambda * 3.0)) errMsg)
executing: drc(TransistorEleEdge activeEdge (sep < (lambda * 2.0)) errMsg)
executing: drc(TransistorEleEdge activeEdge (sep < (lambda * 1.0)) errMsg)
executing: drc(TransistorEleEdge polyEdge (sep < (lambda * 3.0)) errMsg)
executing: drc(TransistorEleEdge polyEdge (sep < (lambda * 2.0)) errMsg)
executing: saveDerived(geomNetTransistorEle (sep < (lambda * 3.0)) errMsg)
executing: saveDerived(geomNetTransistorEle (sep < (lambda * 2.0)) errMsg)
executing: saveDerived(geomNetTransistorEle cs) errMsg)
executing: drc(codEdge (width < (lambda * 2.0)) errMsg)
executing: drc(codEdge (notch < (lambda * 3.0)) errMsg)
executing: drc(codEdge (notch < (lambda * 2.0)) errMsg)
executing: drc(codEdge (area > ((lambda * 2.0 * (lambda * 2.0)) + (lambda * 0.1 * (lambda * 0.1)))) ... errMsg)
executing: drc(CompactEleEdge codEdge (enc < (lambda * 2.0)) errMsg)
executing: saveDerived(geomNetNet("elec") "(SONS Rule 13 3.13.4) electrode enclosure of cont... errMsg)
executing: drc(codEdge polyEdge (sep < (lambda * 3.0)) errMsg)
executing: saveDerived(geomNetNet("elec") "(SONS Rule 13 3.13.4) electrode enclosure of cont... errMsg)
executing: drc(codEdge activeEdge (sep < (lambda * 3.0)) errMsg)
executing: saveDerived(geomNetNet("active") (sep < (lambda * 3.0)) errMsg)
executing: drc(via2Edge (width < (lambda * 2.0)) errMsg)
executing: drc(via2Edge (area > ((lambda * 2.0 * (lambda * 2.0)) + (lambda * 0.1 * (lambda * 0.1)))) ... errMsg)
executing: drc(metal2Edge via2Edge (enc < (lambda * 1.0)) errMsg)
executing: drc(metal2Edge via2Edge (width < (lambda * 5.0)) errMsg)
executing: saveDerived(geomNetNet("via2_metal3") "(SONS Rule 13 3.13.4) electrode enclosure of cont... errMsg)
executing: drc(metal2Edge (sep < (lambda * 3.0)) errMsg)
drc(metal2Edge (notch < (lambda * 3.0)) errMsg)
executing: drc(chipresEdge (width < (lambda * 4.0)) errMsg)
executing: drc(chipresEdge (notch < (lambda * 4.0)) errMsg)
executing: drc(chipresEdge codEdge (sep < (lambda * 2.0)) errMsg)
executing: drc(chipresEdge codEdge (sep < (lambda * 2.0)) errMsg)
executing: saveDerived(geomNetNet("cap") errMsg)
executing: drc(chipresEdge activeEdge (sep < (lambda * 4.0)) errMsg)
executing: saveDerived(geomNetNet("elecHighres") (sep < (lambda * 2.0)) errMsg)
executing: saveDerived(geomNetNet("elecHighres") (sep < (lambda * 2.0)) errMsg)
executing: saveDerived(geomNetNet("elecHighres") (ignore == 2)) errMsg)
executing: saveDerived(geomNetNet("elecHighres") (overall)) "(SONS Rule 27.6) resistor must be outside w... errMsg)
executing: saveDerived(geomNetNet("elecHighres") (overall)) "(SONS Rule 27.6) resistor must be outside w... errMsg)
executing: drc(elelighresEdge (sep < (lambda * 5.0)) errMsg)
drc(elelighresEdge (notch < (lambda * 7.0)) errMsg)
executing: drc(elelighresEdge (width < (lambda * 2.0)) errMsg)
DRC started ... Sun Dec 18 20:35:28 2022
completed ... Sun Dec 18 20:35:28 2022
CPU TIME = 00:00:00 TOTAL TIME = 00:00:00
*****Summary of rule violations for cell "Proj_Clock layout" *****
Total errors Found: 0

```

Figure 31: DRC - Clock

4.7 Proof of Passing LVS

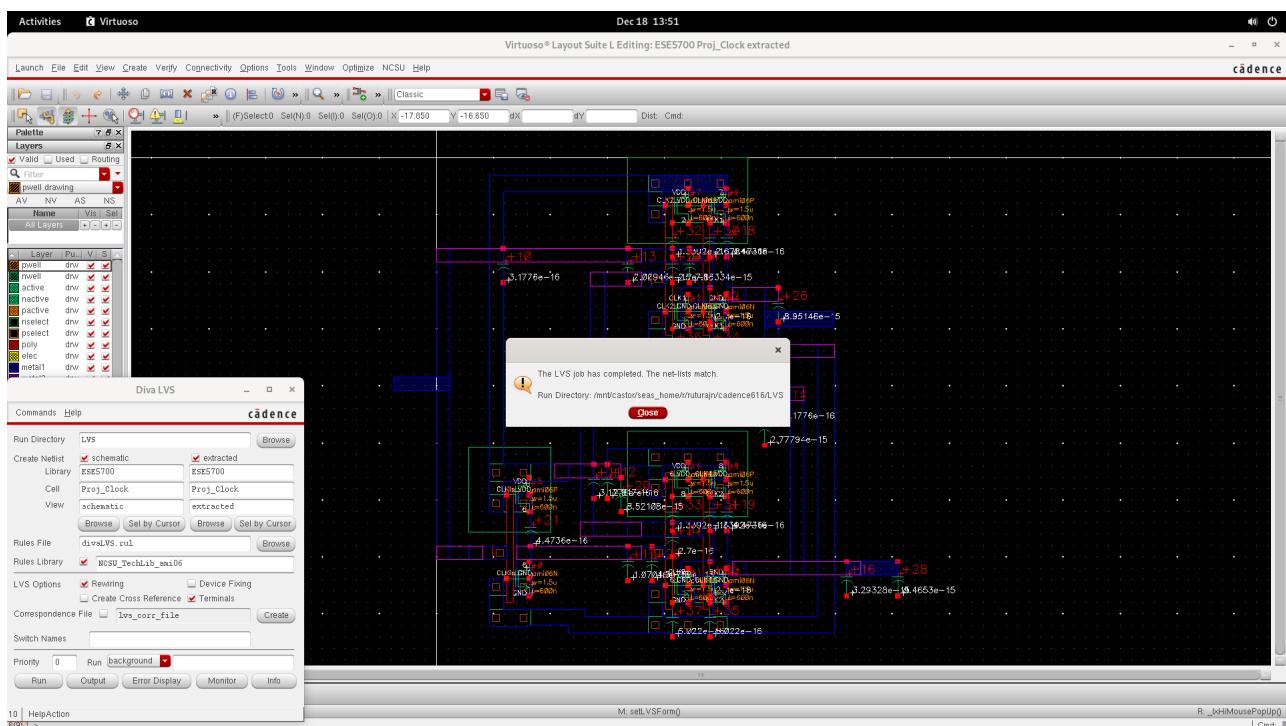


Figure 32: LVS - Clock

```

Activities Virtuoso
Dec 18 13:52
/mnt/castor/seas_home/r/ruturajn/cadence616/LVS/si.out
File Edit View Help
cadence

5      rmos

Terminal correspondence points
N5      N5      CLK1
N4      N4      CLK2
N5      N7      GNDin
N3      N2      GND
N7      N1      VDD

Devices in the netlist but not in the rules:
  popcap
Devices in the rules but not in the netlist:
  cap nfet pfet rmos4 pmos4

The net-lists match.
          layout schematic
instances
un-matched          0      0
reserved           0      0
size errors        0      0
pruned             0      0
active             10     10
total              10     10

nets
un-matched          0      0
merged              0      0
pruned              0      0
active              8      8
total               8      8

terminals
un-matched          0      0
matched but different type  0      0
total               5      5

Probe files from /mnt/castor/seas_home/r/ruturajn/cadence616/LVS/schematic
devbad.out:
netbad.out:
mergenet.out:
terabad.out:
prunenet.out:
prunedev.out:
audit.out:

Probe files from /mnt/castor/seas_home/r/ruturajn/cadence616/LVS/layout
devbad.out:
netbad.out:
mergenet.out:
terabad.out:
prunenet.out:
prunedev.out:
audit.out:

```

Figure 33: LVS Output 1 - Clock

```

Activities Virtuoso
Dec 18 13:52
/mnt/castor/seas_home/r/ruturajn/cadence616/LVS/si.out
File Edit View Help
cadence

R@FUSCUS: LVS version 5.1.6 09/01/2015 15:36 (aifol105) $.
Command line: /mnt/pulux/software/ic-design/cadence/IC616/tools/lrv86/dfl1/bin/32bit/LVS -dir /mnt/castor/seas_home/r/ruturajn/cadence616/LVS -l -s -t /mnt/castor/seas_home/r/ruturajn/cadence616/LVS /mnt/castor/seas_home/r/ruturajn/cadence616/LVS/schematic
Like matching is enabled
Net swapping is enabled
Using 1000000 correspondence points.
Compiling Diffs LVS rules...
Net-list summary for /mnt/castor/seas_home/r/ruturajn/cadence616/LVS/layout/netlist
count
  5      nets
  5      terminals
  5      pmos
  5      rmos

Net-list summary for /mnt/castor/seas_home/r/ruturajn/cadence616/LVS/schematic/netlist
count
  5      nets
  5      terminals
  5      pmos
  5      rmos

Terminal correspondence points
N5      N5      CLK1
N4      N4      CLK2
N5      N7      GNDin
N3      N2      GND
N7      N1      VDD

Devices in the netlist but not in the rules:
  popcap
Devices in the rules but not in the netlist:
  cap nfet pfet rmos4 pmos4

The net-lists match.
          layout schematic
instances
un-matched          0      0
reserved           0      0
size errors        0      0
pruned             0      0
active             10     10
total              10     10

nets
un-matched          0      0
merged              0      0
pruned              0      0
active              8      8
total               8      8

terminals
un-matched          0      0
matched but different type  0      0
total               5      5

Probe files from /mnt/castor/seas_home/r/ruturajn/cadence616/LVS/schematic
devbad.out:
netbad.out:
mergenet.out:
terabad.out:
prunenet.out:
prunedev.out:
audit.out:

```

Figure 34: LVS Output 2 - Clock

5 D FLIP FLOP

5.1 Schematic

We have designed a positive edge triggered D Flip Flop using Pass transistors and inverters. The D Flip Flop is of the Master - Slave configuration. All the transistors used in the design of the D Flip Flop are minimum sized.

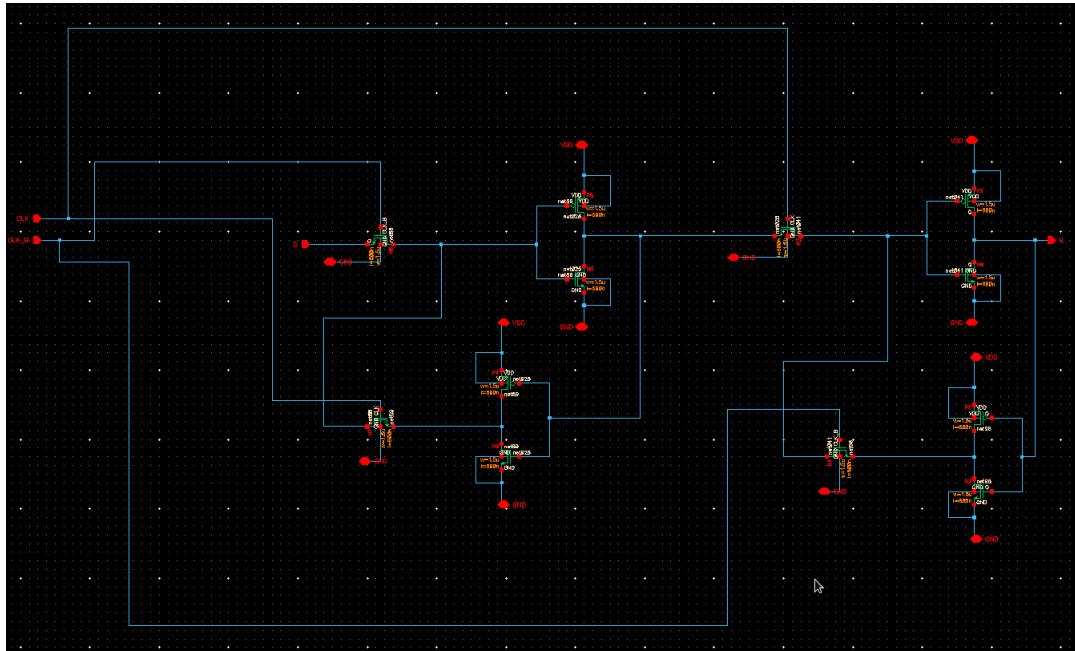


Figure 35: Circuit Schematic for D Flip Flop

5.2 Symbol

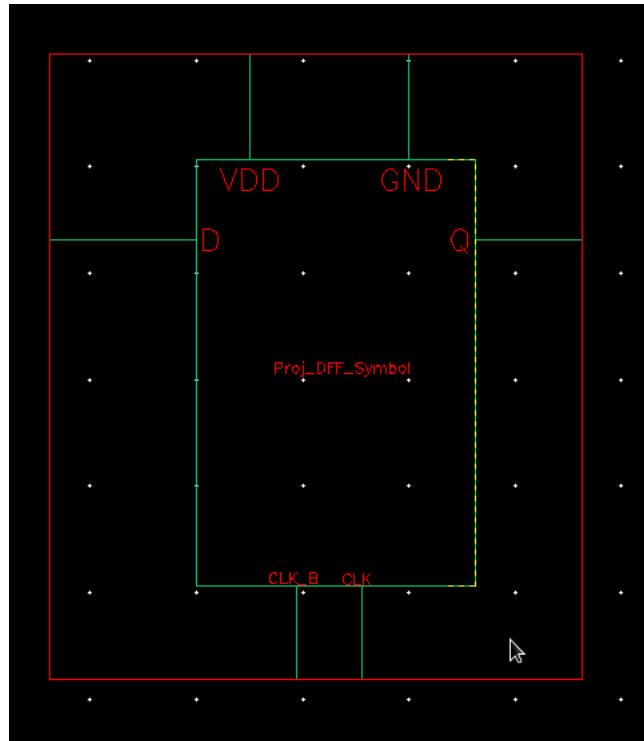


Figure 36: Symbol for D Flip Flop

5.3 Test schematic using Symbol

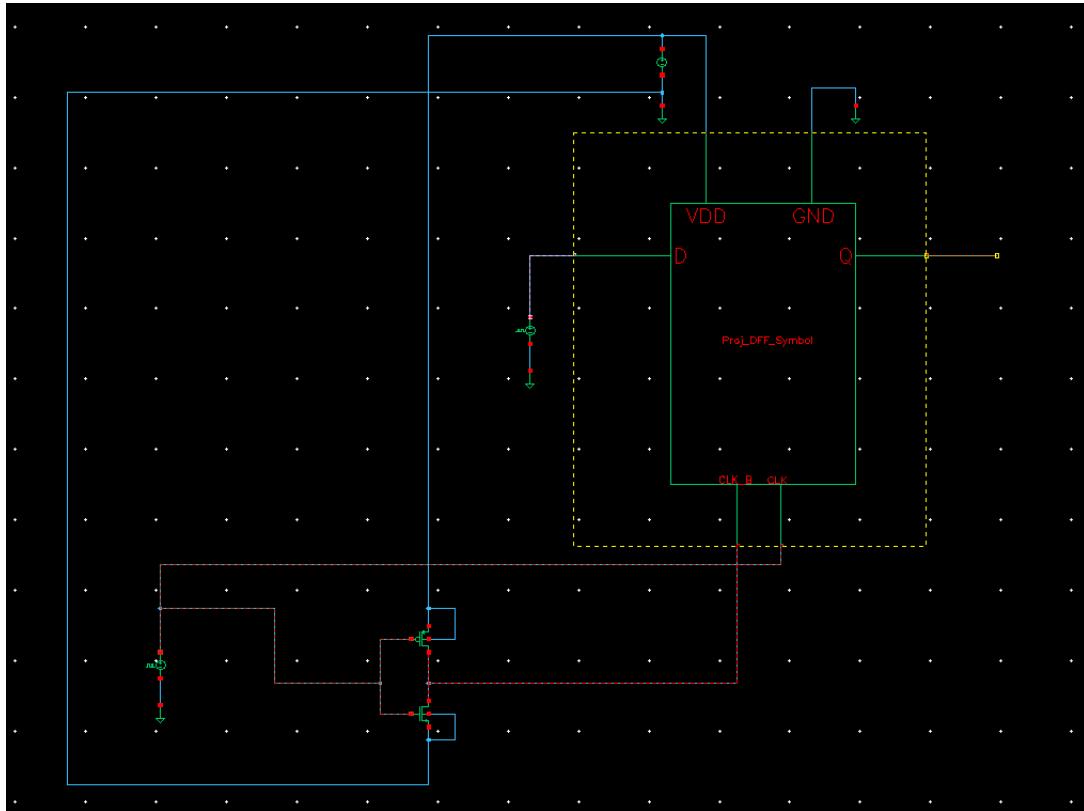


Figure 37: Symbol for D Flip Flop

For testing our D Flip Flop, we provided a *vpulse* to the *CLK*, and its inverted output to *CLK_B*. We have also set a *vpulse* as our input data D.

5.4 Functionality Verification



Figure 38: Functionality Verification for the D Flip Flop

From this plot , it is evident that the output (Q) follows the input data (D) when a positive edge of the clock is encountered since we have designed a positive edge triggered D Flip Flop. This justifies the working of our D Flip Flop.

5.5 Layout

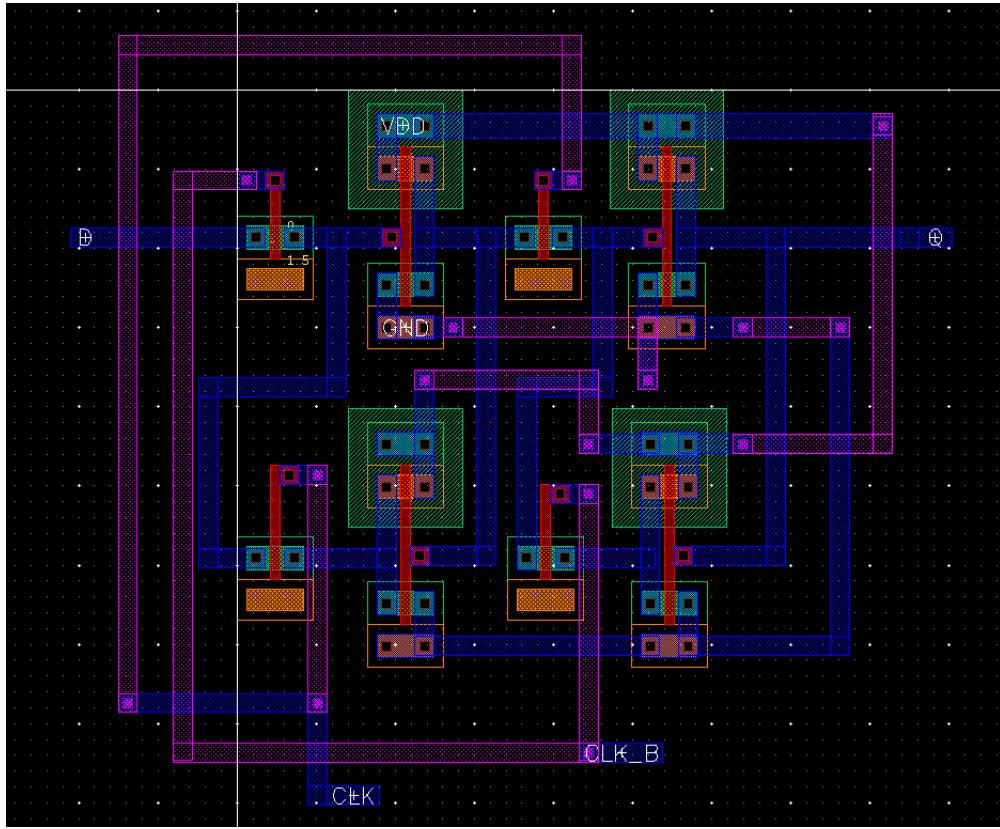


Figure 39: Layout for the D Flip Flop

5.6 Proof of Passing DRC

Figure 40: D Flip Flop - DRC

5.7 Proof of Passing LVS

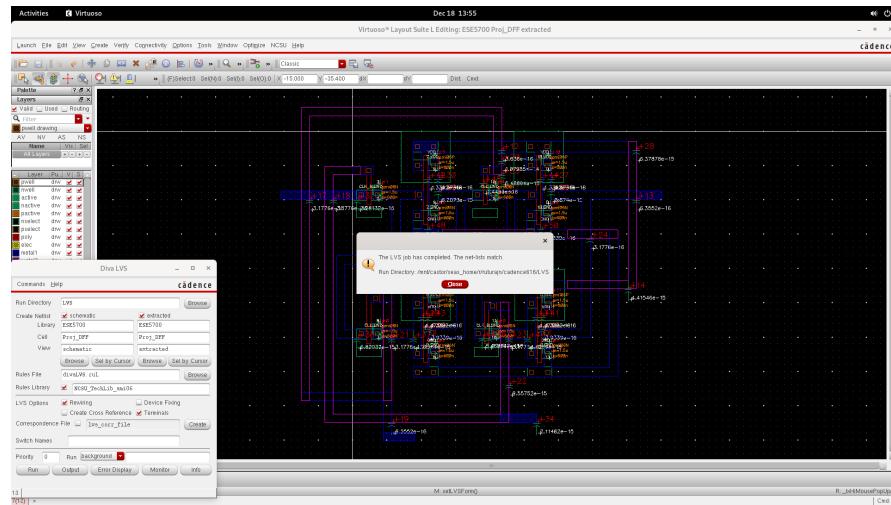


Figure 41: D Flip Flop - LVS

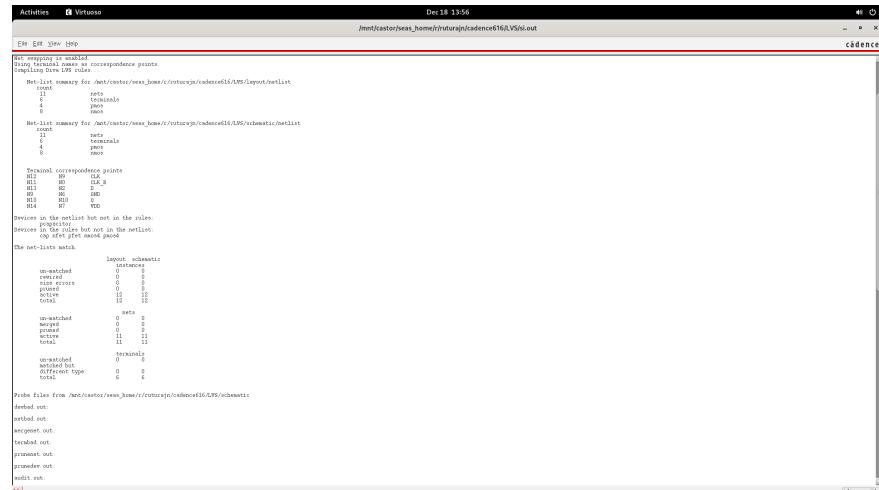


Figure 42: D Flip Flop - LVS Output 1

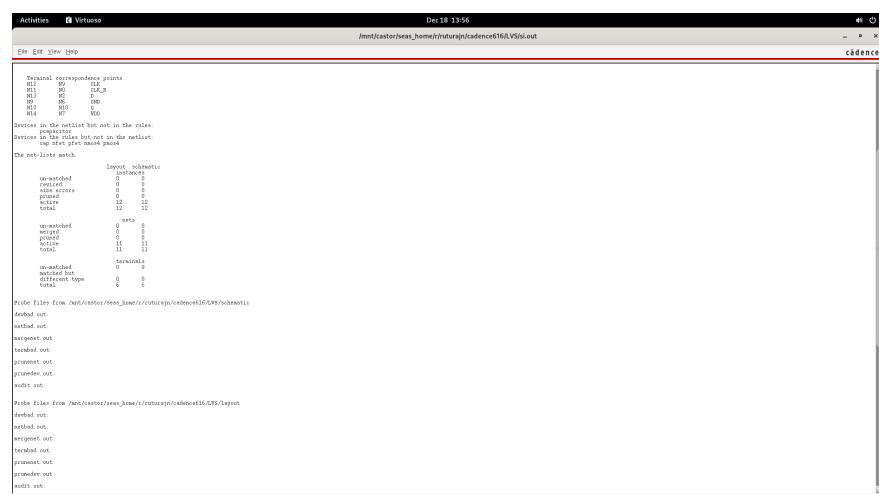


Figure 43: D Flip Flop - LVS Output 2

6 SERIAL IN PARALLEL OUT REGISTER

We are using a serial in parallel out shift register to which we input a serial bitstream . The output from the serial in parallel out shift register is fed to the SRAM array. This is done by cascading 16 D Flip Flops in series. The output at each stage is in parallel given to the SRAM array(16 SRAM's cascaded together).

6.1 Schematic

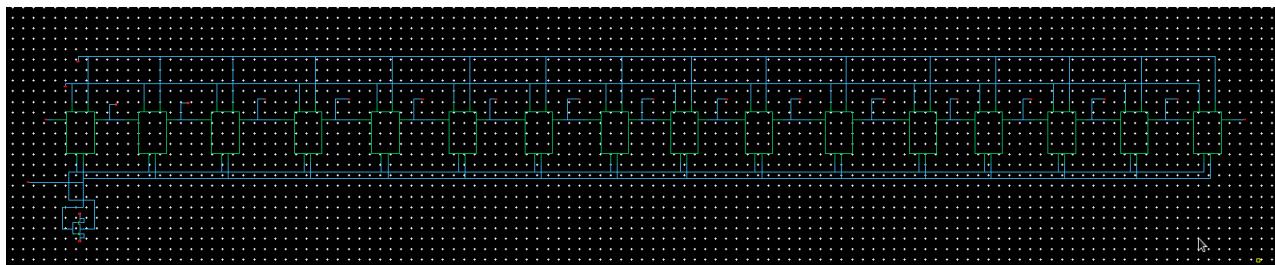


Figure 44: Circuit Schematic - Serial In Parallel Out register

6.2 Symbol

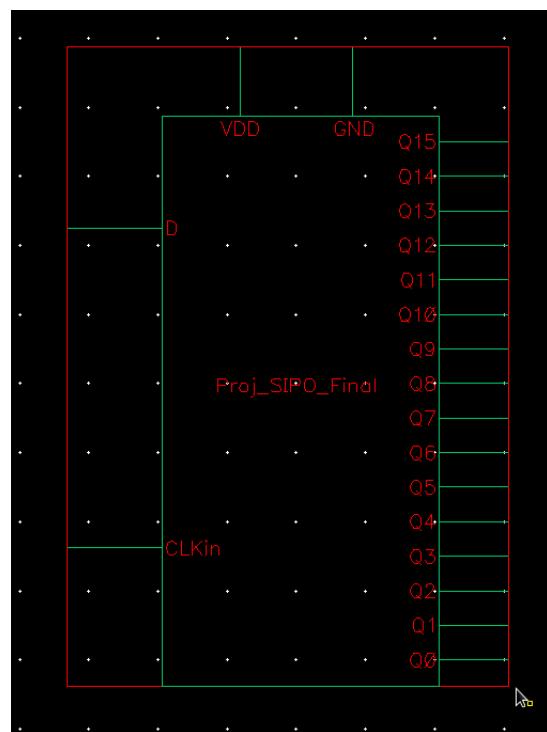


Figure 45: Symbol - Serial In Parallel Out register

6.3 Test schematic using symbol

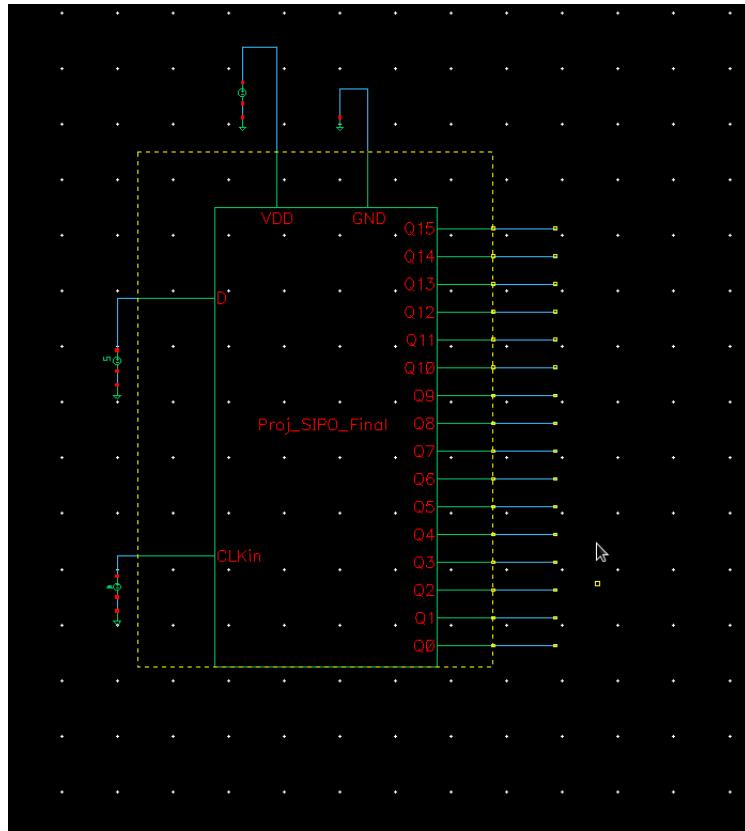


Figure 46: Test Schematic - Serial In Parallel Out register

Fig. 46 shows the test schematic for the Serial In Parallel Out register. The input is fed with a *vbit* source that gives out binary data 1101111010111010.

6.4 Functionality Verification

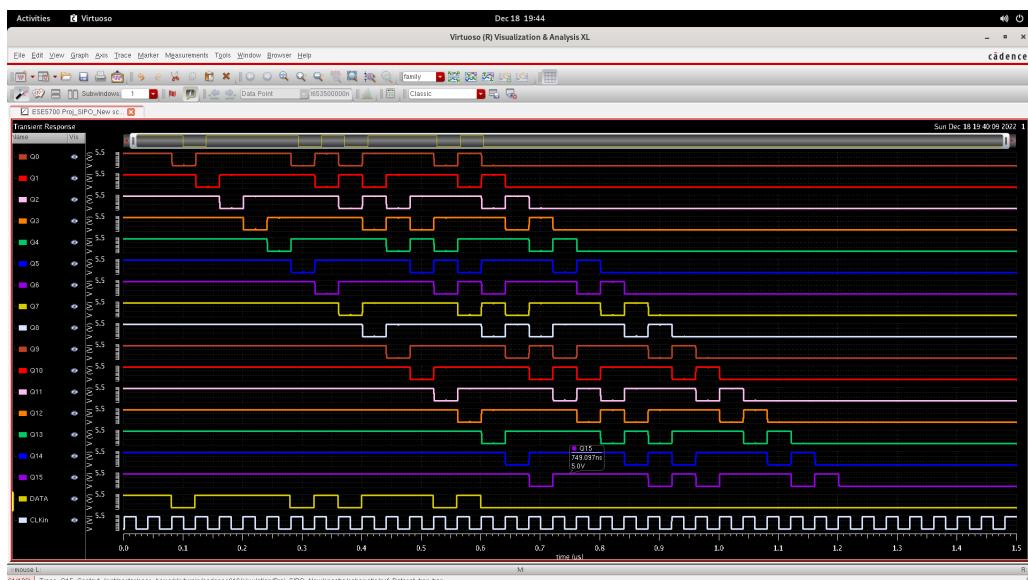


Figure 47: Verification of Functionality - Graph

As expected, Fig. 47 shows the input data being shifted into the register serially, and each bit is available at the output of each flip flop. The output at each stage of the Serial In Parallel Out register is slightly delayed with respect to the stage before it which confirms that the register is working properly.

6.5 Layout

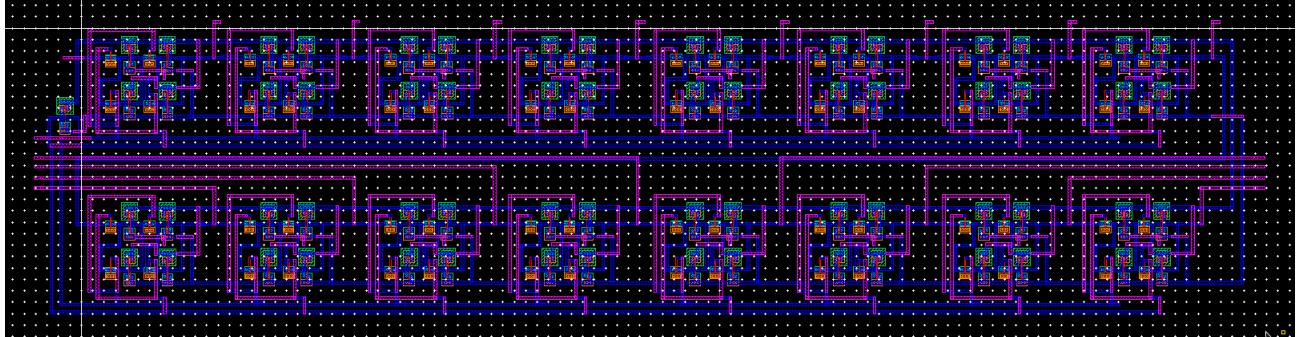


Figure 48: Layout - Serial In Parallel Out register

6.6 Proof of Passing DRC

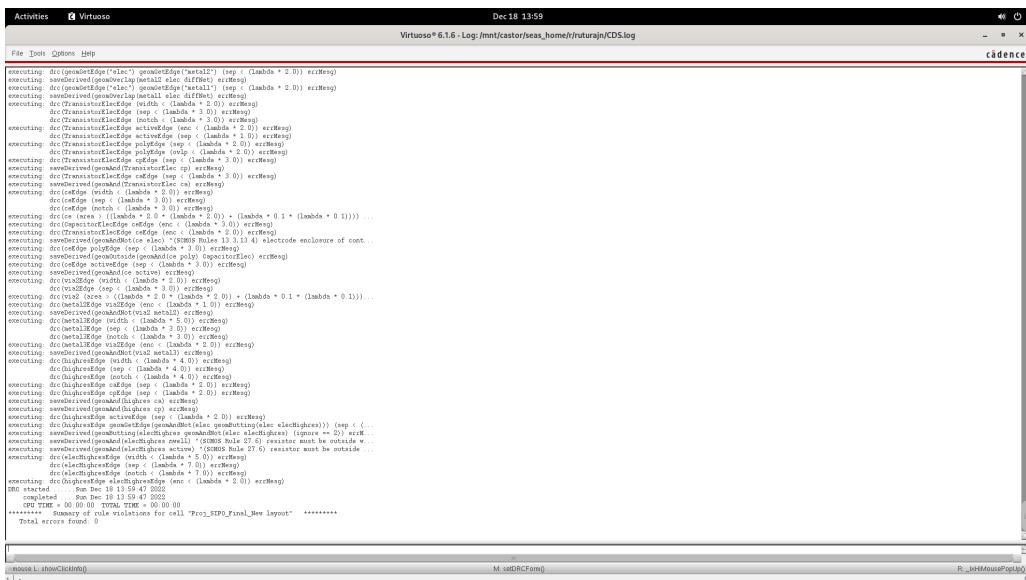


Figure 49: DRC - Serial In Parallel Out register

6.7 Proof of Passing LVS

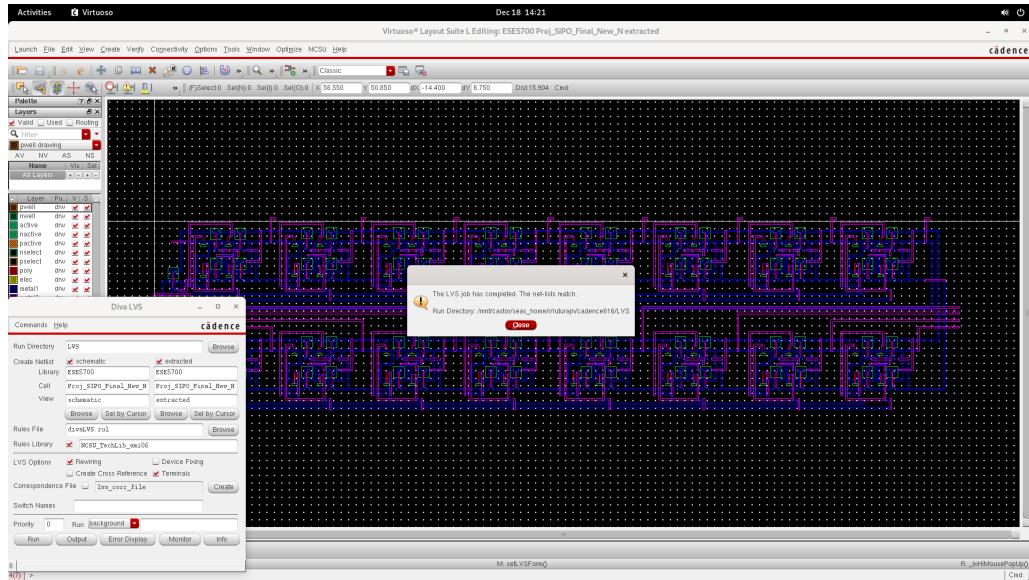


Figure 50: LVS - Serial In Parallel Out register

```
Activities  Virtuoso
Dec 18 14:21
/mnt/castor/seas_home/ruturaj/cadence61b/LVS/si.out
cadence

Edu View Help
#DIVSOS: LVS version 6.1.0 09/01/2011 18:10: (xjfallis) $ 
Command line: /usr/ppl00/nsoftice/ic-design/cadence/lvs6/tools/lxos/dfl1/bin/32bit/LVS -dir /mnt/castor/seas_home/c/ruturaj/cadence61b/LVS -l -t /mnt/castor/seas_home/c/ruturaj/cadence61b/LVS/layout /mnt/castor/seas_home/c/ruturaj/cadence61b/LVS/schematic
Using terminal names as correspondence points.
Correspondence file: /mnt/castor/seas_home/c/ruturaj/cadence61b/LVS/si.out

Net-list summary for /mnt/castor/seas_home/c/ruturaj/cadence61b/LVS/layout.netlist
  count   nets   terminals
  101     0       0
  65     100      100
  120     0       0

Net-list summary for /mnt/castor/seas_home/c/ruturaj/cadence61b/LVS/schematic.netlist
  count   nets   terminals
  101     0       0
  65     100      100
  120     0       0

Terminal correspondence points
W157  W1  Q1X1
W158  W11  Q1D
W159  W11  Q1D
W160  W11  Q1D
W161  W11  Q1D
W162  W11  Q1D
W163  W11  Q1D
W164  W11  Q1D
W165  W11  Q1D
W166  W11  Q1D
W167  W11  Q1D
W168  W11  Q1S
W169  W11  Q1S
W170  W11  Q1S
W957  W11  Q1S
W95
```

```

Activities  Virtuoso
Dec 18 14:21
/mnt/castor/seas_home/c/ruturajn/cadence616/LVS/si.out
cadence

Devices in the netlist but not in the rules:
  programmed
  Devices in the rules but not in the netlist:
  None
The net-lists match.

          layout schematic
un-satched      0
routed          0
size errors     0
pinroute        0
native          194   194
total           194   194

          nets
un-satched      0
mapped          0
printed         101   101
total           101   101

          terminals
un-satched      0
matched but different type  0   0
total           20   20

Probe files from /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/schematic
deshad.out
netbad.out
segment.out
terminal.out
primnet.out
primdev.out
wunit.out

Probe files from /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/Layout
desbad.out
netbad.out
segment.out
terminal.out
primnet.out
primdev.out
wunit.out
$|
```

Figure 52: LVS Output 2 - Serial In Parallel Out register

7 SRAM ARRAY

7.1 Schematic

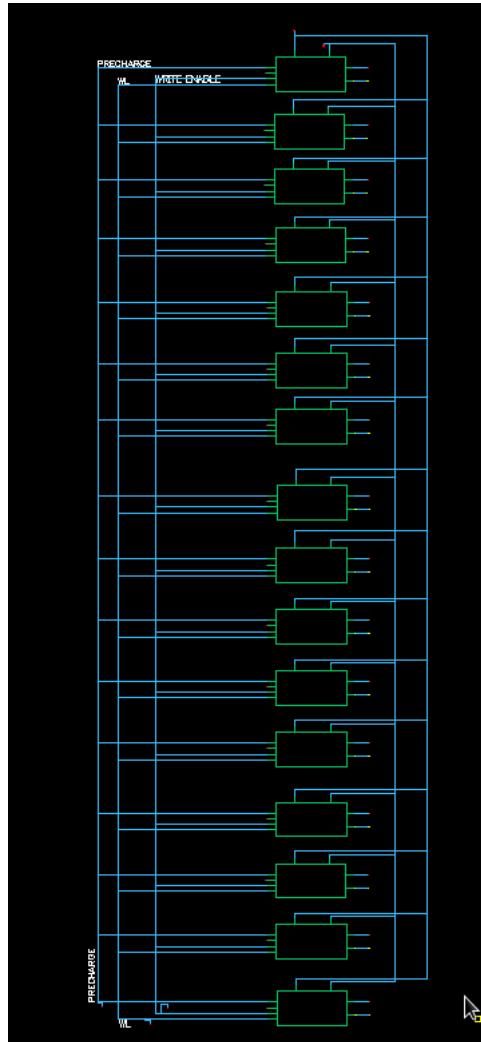


Figure 53: SRAM Array - Schematic

We have designed a SRAM array consisting of 16 SRAM cells cascaded together to feed inputs to the 16:1 Mux. The output BL from each of the individual SRAM cells are connected to the inputs of the 16:1 Mux.

7.2 Symbol

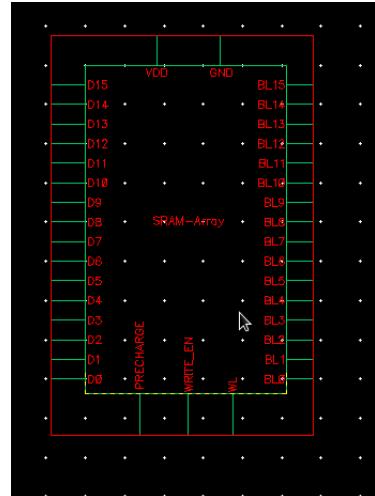


Figure 54: SRAM Array - Symbol

7.3 Test Schematic using symbol

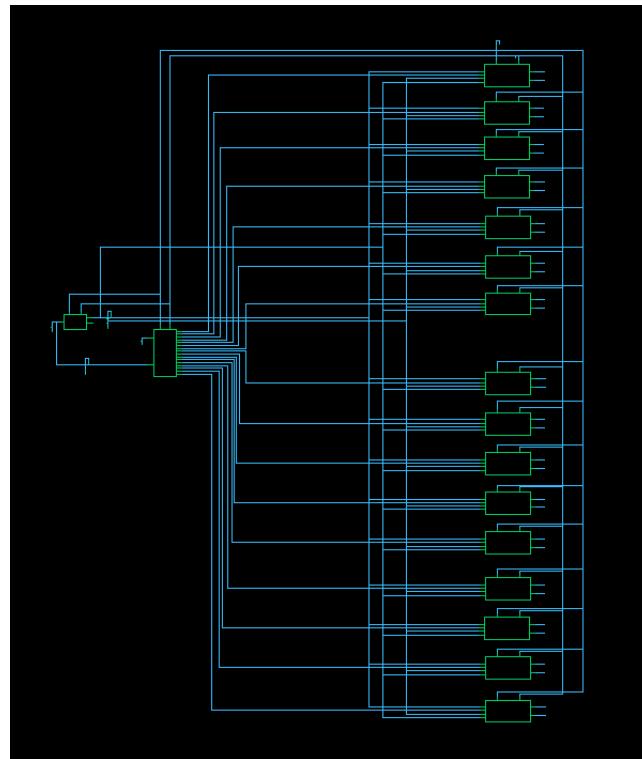


Figure 55: SRAM Array - Test Schematic

The input is fed with a *vbit* source that gives out binary data 1101111010111010. Then the output from the serial in parallel out register is given to each individual SRAM cell in the array.

7.4 Functionality verification

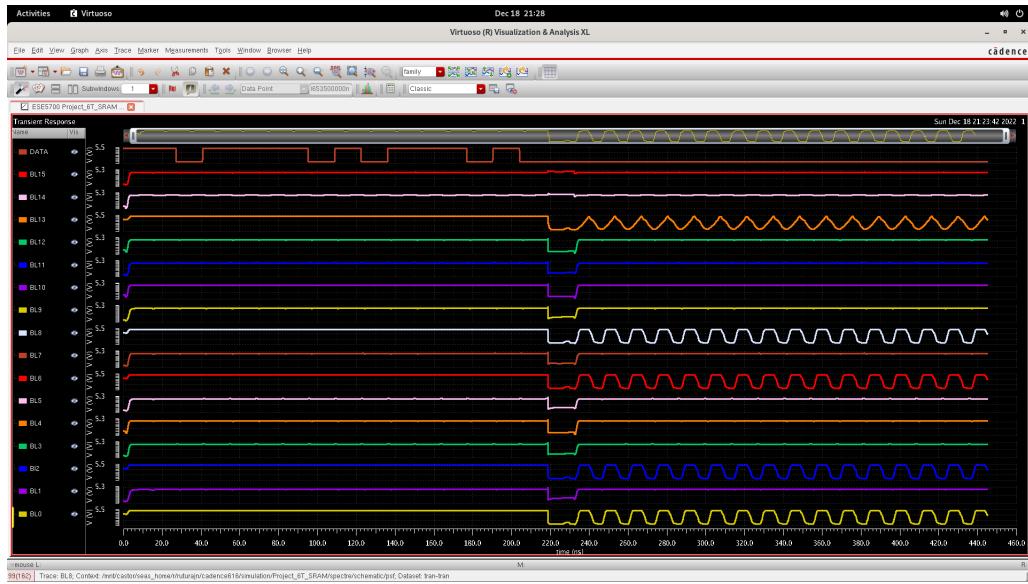


Figure 56: Functionality Verification Graph

Here, we can see that the output at each stage of the SRAM array exactly follows the input data which was fed 1101111010111010 using a vbit source. Reading a 0 produces an oscillating waveform which can be seen in the waveforms. Reading a 1 produces a constant 1. The graph shows that the output replicates the input data and this verifies the functionality of our SRAM array.

7.5 Layout

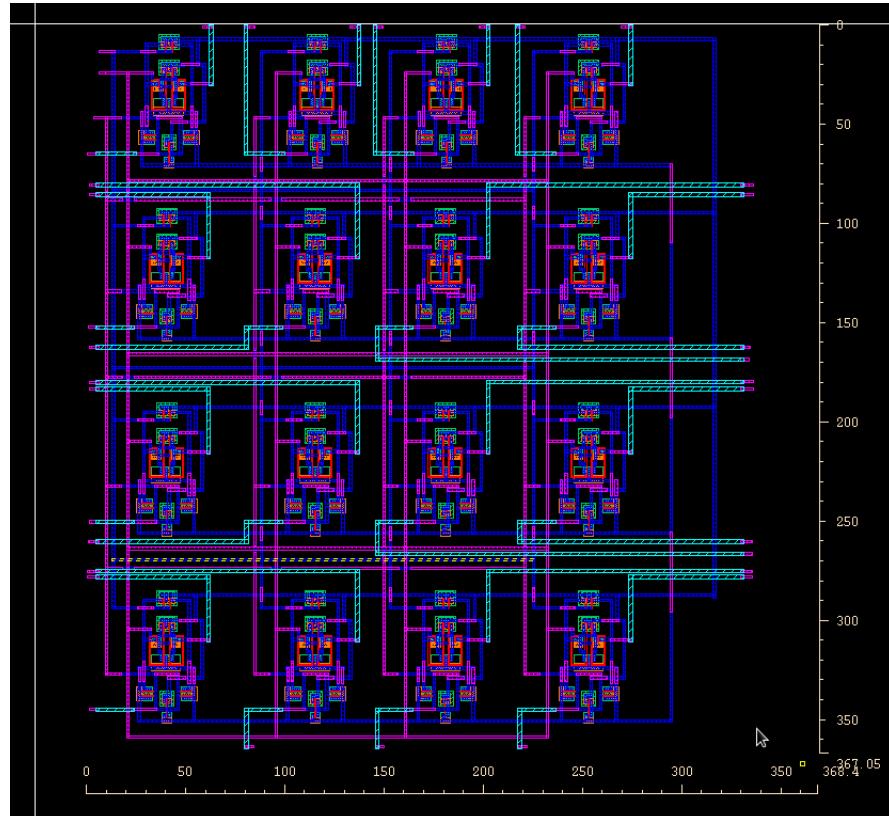


Figure 57: Layout - SRAM Array

7.6 Proof of Passing DRC

Figure 58: DRC - SRAM Array

7.7 Proof of Passing LVS

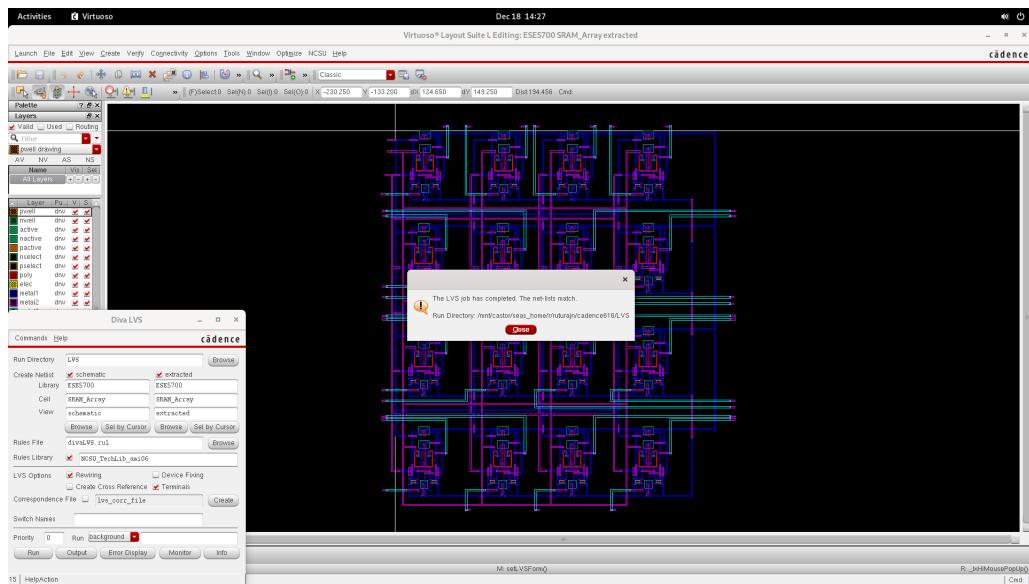


Figure 59: SRAM Array - LVS

```

Activities  | Virtuoso
Dec 18 14:27
/mnt/castor/seas_home/c/ruturajn/cadence616/LVS/si.out
File Edit View Help
#(X)1000: LVS Version 6.1.6 09/01/2015 15:38 (sjf01125) 8
Command line: /opt/pnlun/software/cd-cadence/lvs/tools/lx09v/dfl/bin/ldbt/LVS -dir /mnt/castor/seas_home/c/ruturajn/cadence616/LVS -l -o -t /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/Layout /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/schematic
Link analysis: 0 nodes
Net swapping: it enabled
Duplicating nets: 0
Correspondence points: 0
Compiling DRC LVS rules...
Net-list summary for /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/layout/netlist
nodes 123
nets 123
terminals 123
pins 123
ports 123
DB68 123
144 144

Net-list summary for /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/schematic/netlist
nodes 123
nets 123
terminals 123
pins 123
ports 123
DB68 123
144 144

Terminal correspondence points
N143 N5 H1
N143 N6 H10
N155 N51 H11
N155 N52 H12
N155 N53 H13
N155 N54 H14
N155 N55 H15
N128 N7 H15
N142 N8 H16
N141 N9 H13
N140 N10 H14
N138 N5 H15
N134 N6 H17
N129 N7 H15
N111 N60 H19
N152 N5 H1
N149 N81 H11
N146 N82 H12
N147 N83 H13
N145 N85 H14
N145 N33 H15
N151 N12 H16
N160 N17 H13
N150 N18 H14
N158 N46 H5
N157 N47 H5
N156 N14 H7
N155 N15 H8
N154 N13 H9
N150 N20 PREGND/NVDD
N159 N21 VDD
N154 N51 VDD
N152 N51 VDD
N153 N59 MNTRX_XN
N153 N60 MNTRX_XN

Devices in the netlist but not in the rules:
programmed
Devices in the rules but not in the netlist:
cap net pfet nand4 pmos4

The net-lists match:
      layout schematic
      instances instances
un-matched      0      0
reserved      0      0
  
```

Figure 60: SRAM Array - LVS Output 1

```

Activities  | Virtuoso
Dec 18 14:27
/mnt/castor/seas_home/c/ruturajn/cadence616/LVS/si.out
File Edit View Help
#(X)1000: LVS Version 6.1.6 09/01/2015 15:38 (sjf01125) 8
Command line: /opt/pnlun/software/cd-cadence/lvs/tools/lx09v/dfl/bin/ldbt/LVS -dir /mnt/castor/seas_home/c/ruturajn/cadence616/LVS -l -o -t /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/Layout /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/schematic
Link analysis: 0 nodes
Net swapping: it enabled
Duplicating nets: 0
Correspondence points: 0
Compiling DRC LVS rules...
Net-list summary for /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/layout/netlist
nodes 123
nets 123
terminals 123
pins 123
ports 123
DB68 123
144 144

Net-list summary for /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/schematic/netlist
nodes 123
nets 123
terminals 123
pins 123
ports 123
DB68 123
144 144

Terminal correspondence points
N157 N15 DB
N156 N16 DB
N155 N64 DB
N154 N65 DB
N150 N61 DND
N159 PREGND/NVDD
N154 N55 VDD
N155 N56 NVDD
N153 N59 MNTRX_XN
N153 N60 MNTRX_XN

Devices in the netlist but not in the rules:
programmed
Devices in the rules but not in the netlist:
cap net pfet nand4 pmos4

The net-lists match:
      layout schematic
      instances instances
un-matched      0      0
reserved      0      0
  
```

Figure 61: SRAM Array - LVS Output 2

8 CONFIGURABLE LOGIC BLOCK

8.1 Schematic

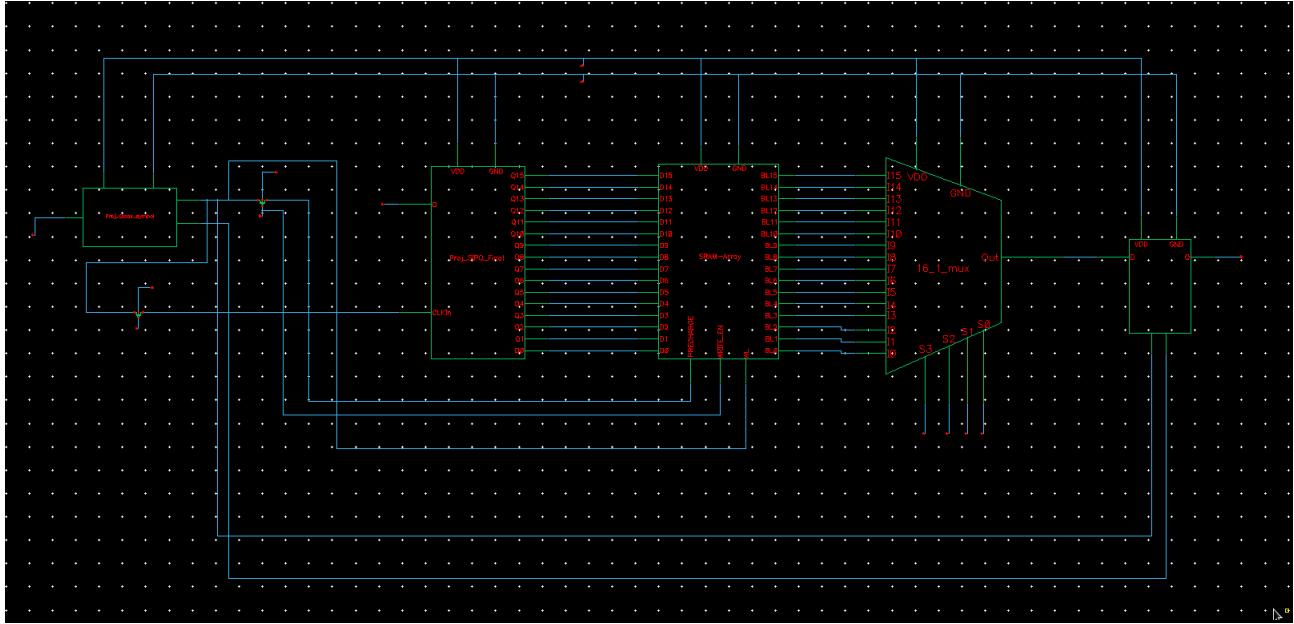


Figure 62: Circuit Schematic for Configurable Logic Block

This schematic represents our Configurable Logic Block and consists of all the individual components that have been designed. The clock module is connected to the Serial In Parallel Out register, to which a serial bitstream is fed. A *LOAD* signal is used to control the Serial In Parallel Out register, which as the name suggests helps us load data into the SIPO 16-bits at a time (i.e. we can switch the state of the Serial In Parallel Out register).

The output from the Serial In Parallel Out register is then given to our SRAM array, which stores the incoming data. Now that the data is stored in the SRAM array, any individual cell is read based on the select inputs of our 16:1 Mux. Finally, to eliminate transients a D Flip Flop is placed at the output.

All the pass transistors used in this schematic(Fig. 62) are minimum sized.

8.2 Symbol

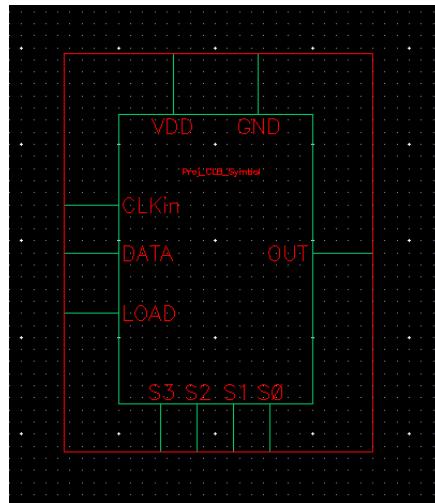


Figure 63: Symbol for Configurable Logic Block

8.3 Functionality at Maximum Frequency

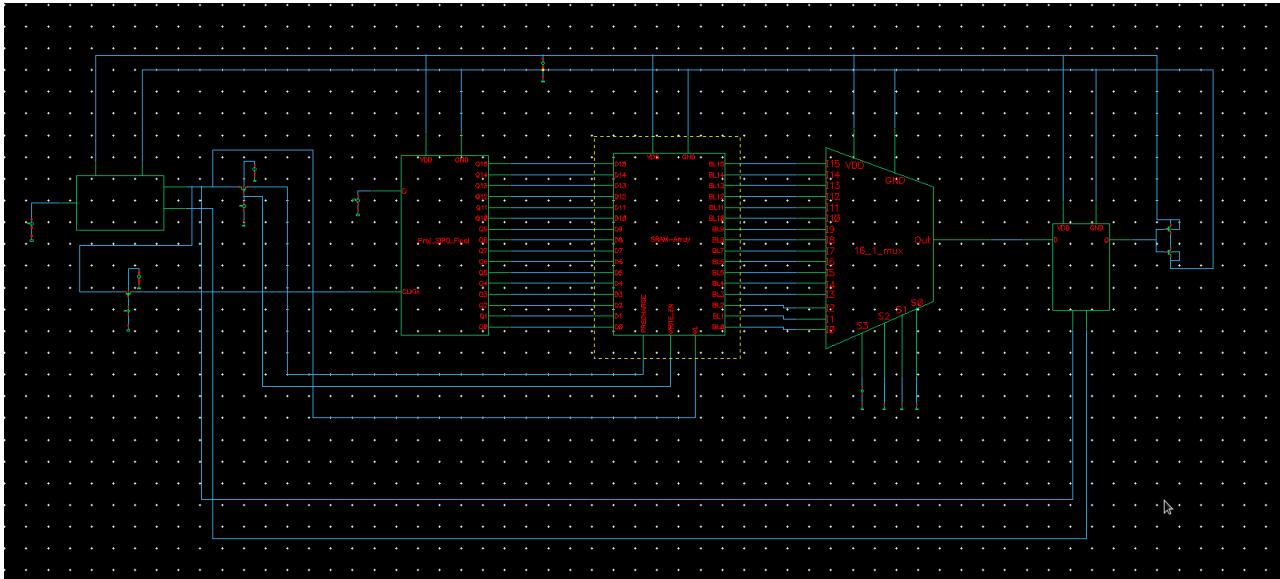


Figure 64: Test Schematic for Maximum Frequency

Verification plot



Figure 65: Verification of the Configurable Logic Block at Maximum Operating Frequency

Fig. 65 indicates that the output follows the input data provided using a *vbit* source depending on the state of the select lines of our 16:1 Mux. The address bits for the LUT are cycled through using *vpulse* sources with varying periods to make sure every combination of the select lines are tested.

We tested the Configurable Logic block for varying periods of CLK_{in} , however, it failed to operate below a time period of 13.6ns. Thus, we had to settle at a time period of 13.6ns for our main clock. This implies that the Maximum operating frequency that our Configurable Logic block operates at is 73.529MHz.

We could have attained higher operating frequency for our Configurable Logic block had we increased the sizes of transistors for most of our components. Since, our SRAM and 16:1 Mux are

not sized to a huge extent , our maximum operating frequency is slightly low, however, this was a conscious design choice keeping in the mind the area that our Configurable Logic block will take.

8.4 Layout

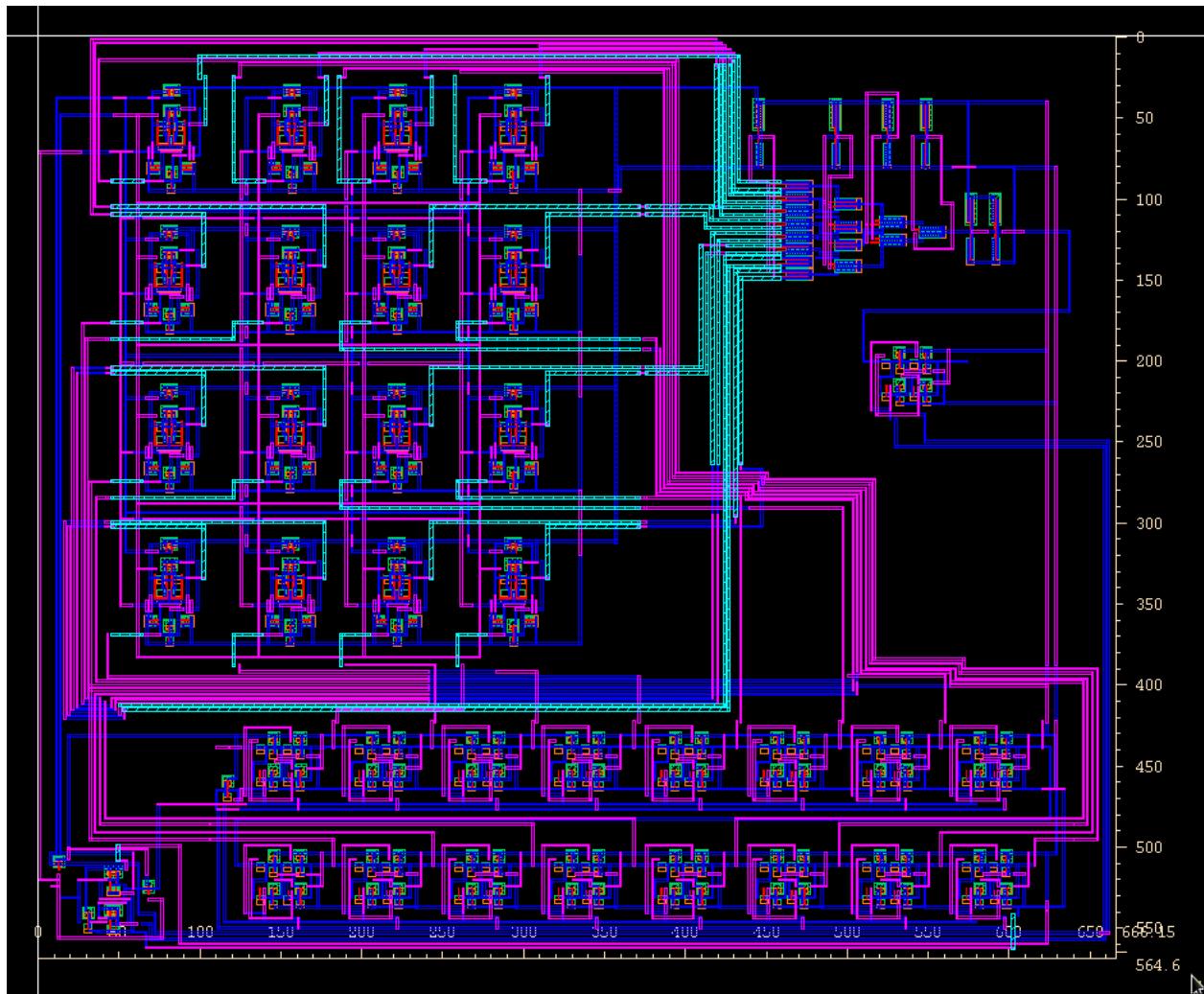


Figure 66: Complete Layout of the Configurable Logic Block

8.5 Proof of Passing DRC

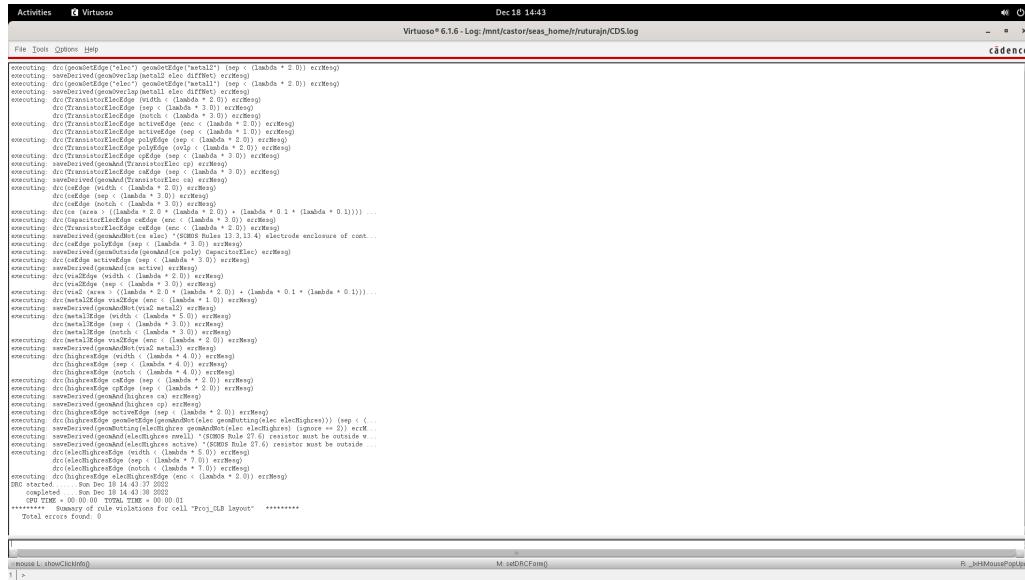


Figure 67: DRC for the Configurable Logic Block

8.6 Proof of Passing LVS

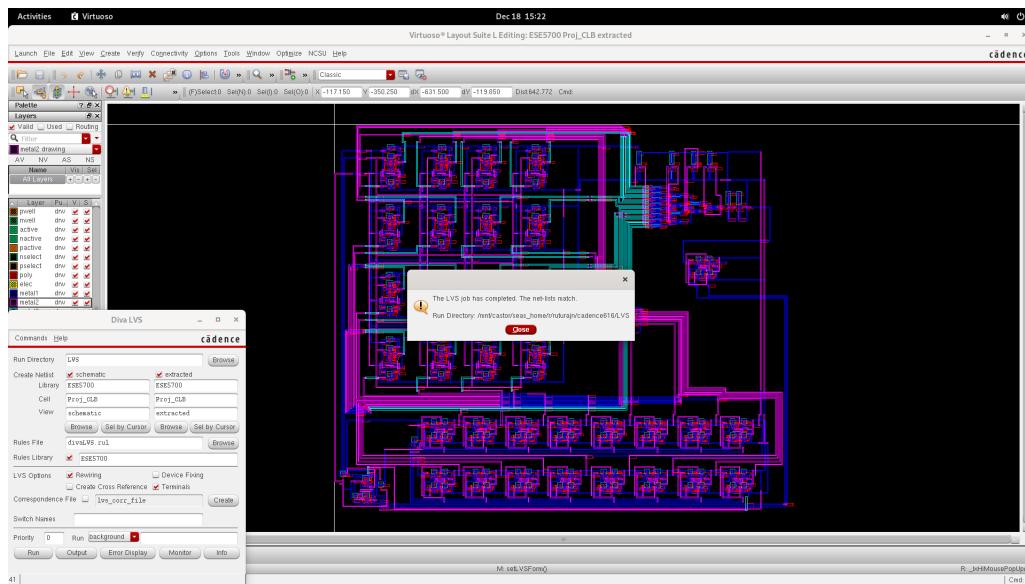


Figure 68: LVS - Configurable Logic Block

```

Activities  Virtuoso
Dec 18 15:23
/mnt/castor/seas_home/c/ruturajn/cadence616/LVS/si.out

LVS Version 6.1.6 09/01/2015 15:38 (sjfcl125) 8
Command line: /opt/pnlun/software/cadence/lolsis/tools.lx09/df11/bin/Dbit/LVS -dir /mnt/castor/seas_home/c/ruturajn/cadence616/LVS -l -o -t /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/Layout /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/schematic
Net mapping is enabled
Dont care points will be correspondence points
Net-list summary for /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/Layout/netlist
  count      nets    terminals
  202        0       162
  162        1       162
  322        2       322
  322        3       322

Net-list summary for /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/schematic/netlist
  count      nets    terminals
  202        0       162
  162        1       162
  322        2       322
  322        3       322

Terminal correspondence points
  N354  N34  GND
  N355  N34  VDD
  N351  N35  GND
  N350  N35  VDD
  N352  N46  GND
  N353  N46  VDD
  N358  N44  S1
  N359  N44  S2
  N360  N45  S3
  N361  N45  S4
  N362  N46  S5
  N363  N46  S6
  N364  N47  S7
  N365  N48  VDD

Devices in the netlist but not in the rules:
  probeout
  Device in the rules but not in the netlist:
  cap net pfet nacod pwoe
The net-lists match

  layout schematic
  instances
  un-watched      0      0
  rewired        0      0
  site errors    0      0
  printed        0      0
  active         484    484
  total          484    484

  nets
  un-watched      0      0
  merged         0      0
  printed        0      0
  total          252    252

  terminals
  un-watched      0      0
  rewired        0      0
  site errors    0      0
  different type  0      0
  total          10    10

Probe file from /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/schematic
deadbad.out:
pathbad.out:
ascrgnet.out:
terabad.out:
42]

```

Figure 69: LVS Output 1 - Configurable Logic Block

```

Activities  Virtuoso
Dec 18 15:23
/mnt/castor/seas_home/c/ruturajn/cadence616/LVS/si.out

N351  N34  DATA
N352  N34  VDD
N360  N5  LOAD
N361  N5  DOUT
N359  N15  GND
N358  N15  VDD
N357  N36  S1
N356  N36  S2
N355  N4  VDD

Devices in the netlist but not in the rules:
  probeout
  Device in the rules but not in the netlist:
  cap net pfet nacod pwoe
The net-lists match

  layout schematic
  instances
  un-watched      0      0
  rewired        0      0
  site errors    0      0
  printed        0      0
  active         484    484
  total          484    484

  nets
  un-watched      0      0
  merged         0      0
  printed        0      0
  active         252    252
  total          252    252

  terminals
  un-watched      0      0
  rewired        0      0
  site errors    0      0
  different type  0      0
  total          10    10

Probe file from /mnt/castor/seas_home/c/ruturajn/cadence616/LVS/schematic
deadbad.out:
pathbad.out:
ascrgnet.out:
terabad.out:
printednet.out:
printeddev.out:
sudit.out:
42]

```

Figure 70: LVS Output 2 - Configurable Logic Block

9 DESIGN METRICS

All our simulations are done using the **Analog Extracted Design**. This includes all the components:

- 16:1 Mux
- SRAM Cell
- Clock
- D Flip Flop
- Serial In Parallel Out Register
- SRAM Array
- Configurable Logic Block

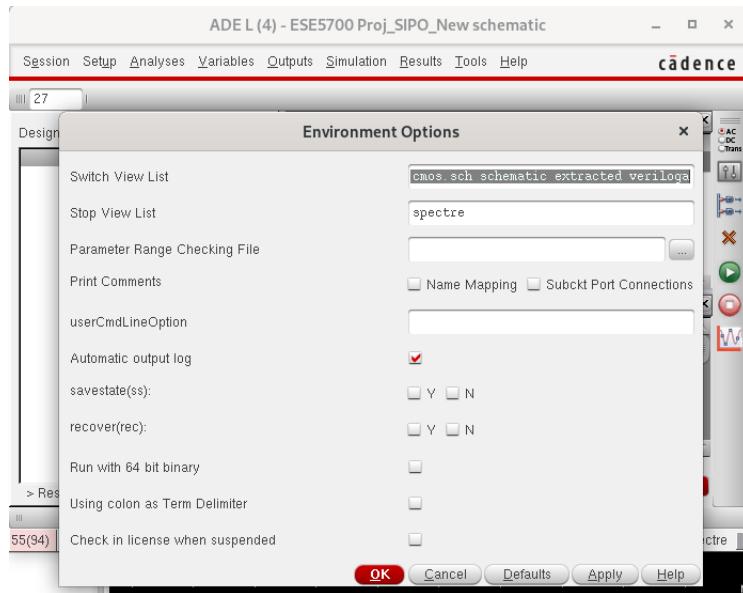


Figure 71: Use of Analog Extracted Design

Fig. 71 shows that we have used the *Analog Extracted Design* for testing functionality. The same has been done for each component of the Configurable Logic Block and the CLB itself as mentioned above.

9.1 Energy

Following are the design metrics for the Configurable Logic Block, namely the loading energy and the active energy.

9.1.1 Loading Energy

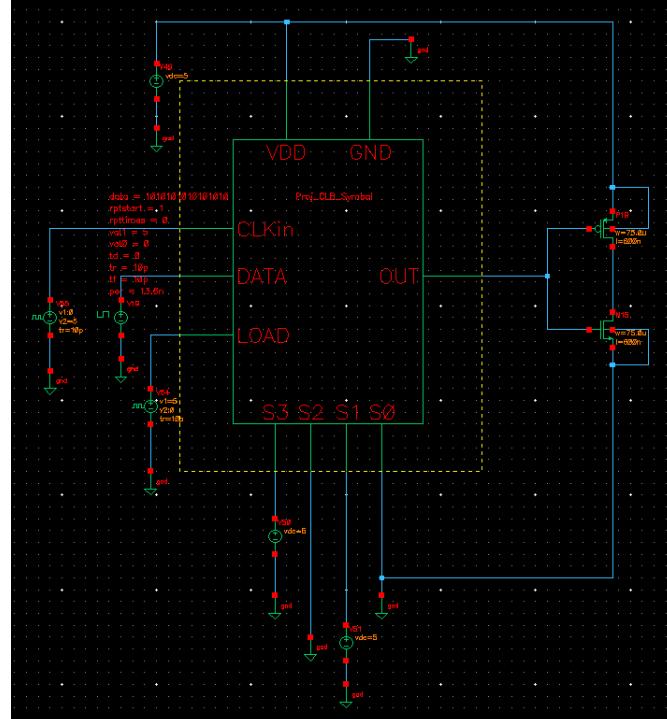


Figure 72: Loading Energy Test Schematic

For measuring the Loading Energy we probed the *VDD* pin of the Serial In Parallel Out register and the SRAM array. Then, the current obtained from the graph was integrated over a time period of 17 cycles (16 cycles for loading our data into the Serial In Parallel Out register and another to write the data into the SRAM array). Finally, the value of energy obtained from both the plots were summed up to give us the total loading energy. Also, the output is loaded with $100C_g$, as mentioned in the handout, for which we have used an inverter with the widths of the PMOS and the NMOS set to $75\mu\text{m}$.

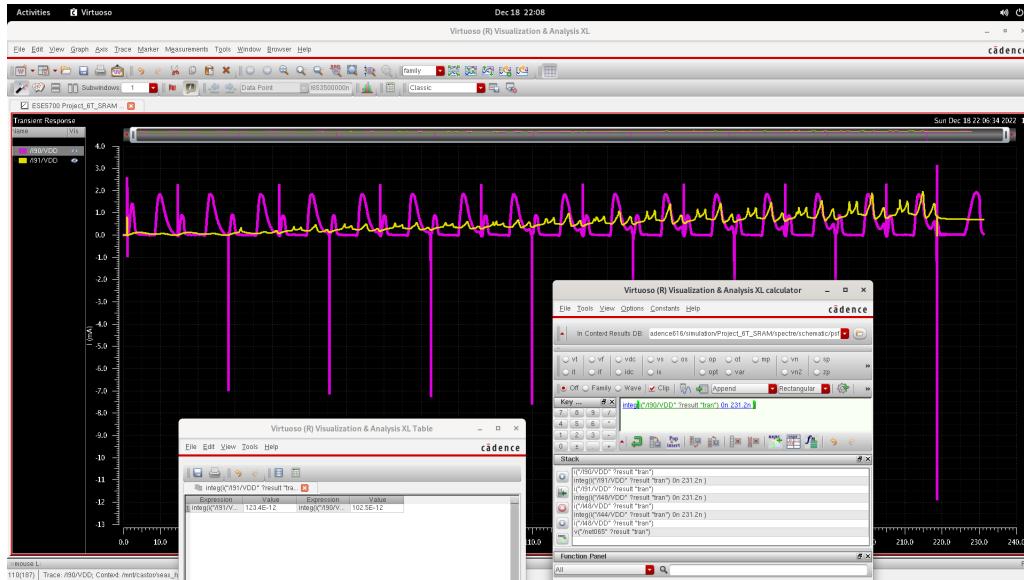


Figure 73: Loading Energy - Current Value calculation



Figure 74: Loading Energy Calculation Graph

9.1.2 Active Energy

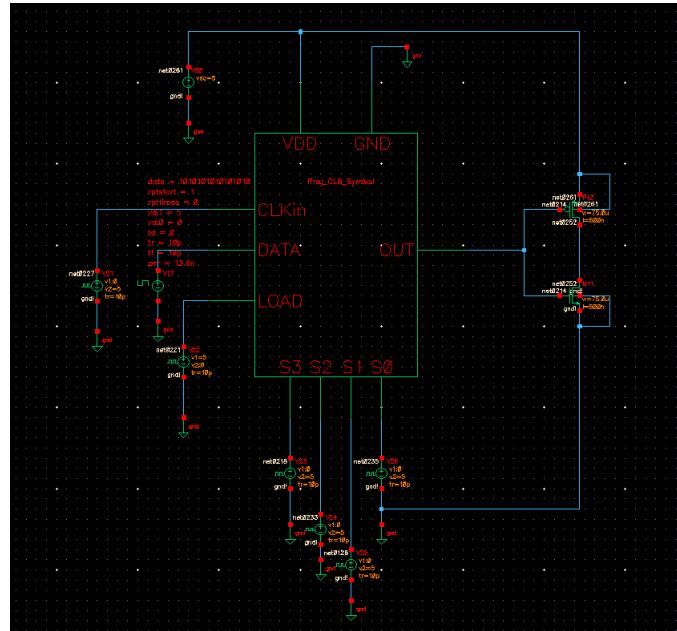


Figure 75: Test Schematic for measuring Active Energy

For measuring the Active Energy we probed the VDD pin of the complete Configurable Logic Block and all the 16 inputs of the LUT. Then, the current obtained from the graph was integrated over a time period of 33 cycles (16 cycles for loading our data into the Serial In Parallel Out register and another to write the data into the SRAM array, finally 16 more to cycle through all the select lines/address bits). Finally, the value of energy obtained from all the plots were summed up to give us the total active energy.

Also, the output is loaded with $100C_g$ as mentioned in the handout, for which we have used an inverter with the widths of the PMOS and the NMOS set to $75\mu\text{m}$.


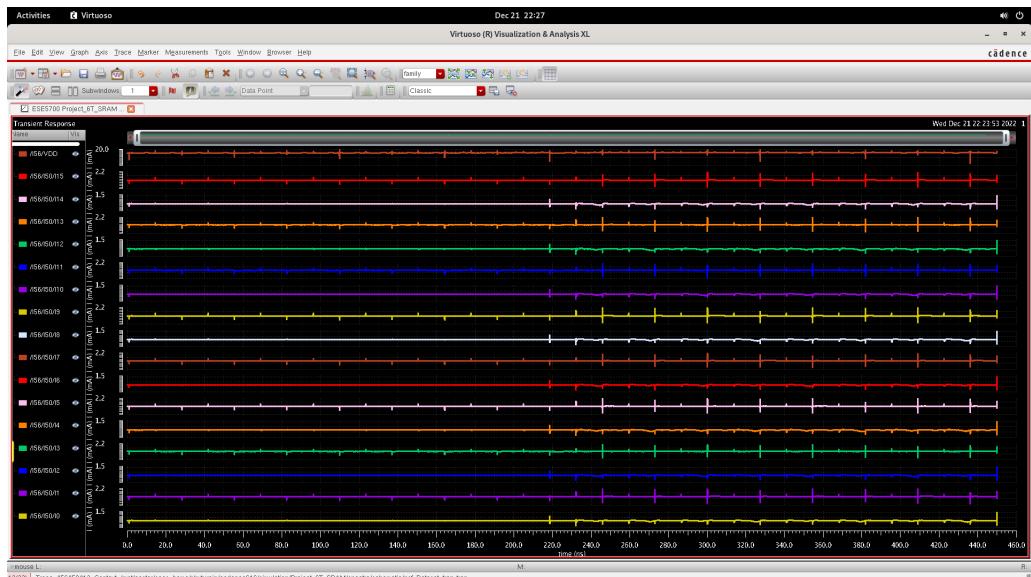



Figure 76: Current Plot

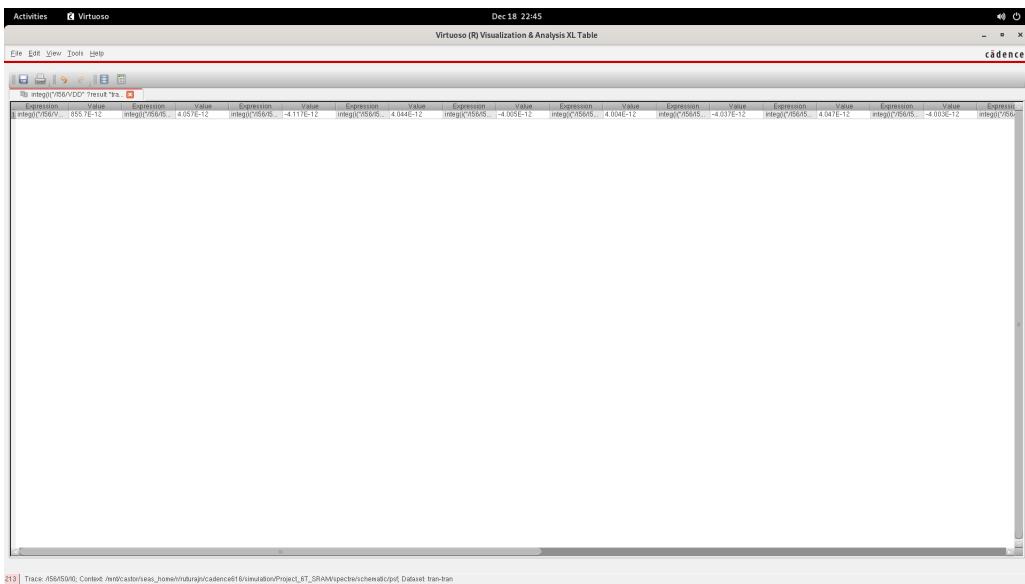

The screenshot shows a Cadence Virtuoso R Visualizer window titled "Virtuoso (R) Visualization & Analysis XL.Table". The table has columns labeled "Expression" and "Value" repeated 16 times. The first few rows of data are as follows:

Expression	Value	Expression	Value	Expression	Value	Expression	Value	Expression	Value	Expression	Value	Expression	Value	Expression	Value	Expression	Value
$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	655.7E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.057E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.117E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.044E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.056E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.037E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.056E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.047E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.036E-12
$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	655.7E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.057E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.117E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.044E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.056E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.037E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.056E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.047E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.036E-12

Figure 77: Current Integral values for some of the plots - 1

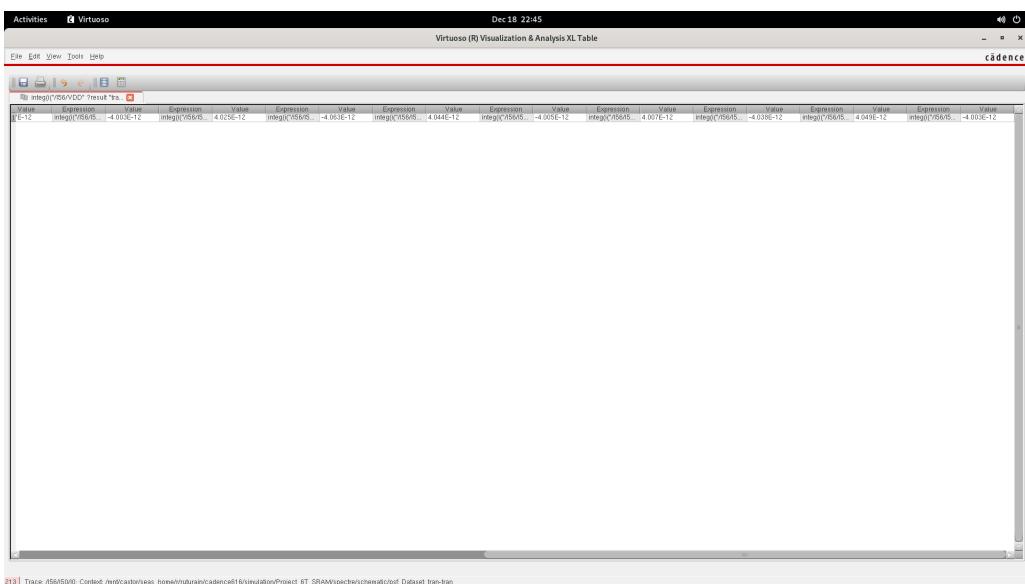

The screenshot shows a Cadence Virtuoso R Visualizer window titled "Virtuoso (R) Visualization & Analysis XL.Table". The table has columns labeled "Expression" and "Value" repeated 16 times. The first few rows of data are as follows:

Expression	Value	Expression	Value	Expression	Value												
$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	655.7E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.036E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.025E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.062E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.044E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.056E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.037E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.036E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.049E-12
$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	655.7E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.036E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.025E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.062E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.044E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.056E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.037E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	-4.036E-12	$\int \text{integ}(VDD/VDD) \cdot \text{result} * t_s$	4.049E-12

Figure 78: Current Integral values for some of the plots - 2

9.1.3 Average Energy

The Loading Energy for our Design is given by,

$$\text{LoadingEnergy} = (\int I) \times V_{DD} = (123.4\text{pA} + 102.5\text{pA}) \times 5 = 1129.5\text{pJ}$$

The Active Energy for our Design is,

$$\text{ActiveEnergy} = (\int I) \times V_{DD} = (\dots + 4.003\text{pA}) \times 5 = 4601.24\text{pJ}$$

Therefore the Average energy is,

$$AverageEnergy = (0.8 \times ActiveEnergy) + (0.2 \times LoadingEnergy)$$

$$AverageEnergy = (0.8 \times 4601.24pJ) + (0.2 \times 1129.5pJ)$$

$$AverageEnergy = 3680.992pJ + 225.9pJ$$

$$AverageEnergy = 3906.892pJ$$

9.2 Maximum Operating Frequency

The max operating frequency that we obtained was **73.529 MHz**, which was based on our time period of $13.6ns$ at which our main clock is operating.

9.3 Figure of Merit

The area that we obtained for the whole CLB was $(666.15 \times 666.15)\mu m^2$. Hence, our FOM turns out to be,


$$FOM = \text{area} \times \text{averageEnergy} \times \frac{1}{\text{maxFrequency}}$$
$$FOM = (666.15 \times 666.15)\mu m^2 \times 3906.892pJ \times \frac{1}{73.529MHz}$$
$$FOM = 2.3578 \times 10^{-23}m^2Js$$

9.4 Summary Table

Max. Operating Frequency	Area	Average Energy
73.529MHz	$(666.15 \times 666.15)\mu m^2$	3906.892pJ

APPENDIX : REPRESENTATION OF ELMORE DELAY FOR THE LUT

Stage 1 - Input Drive for 16:1 Mux

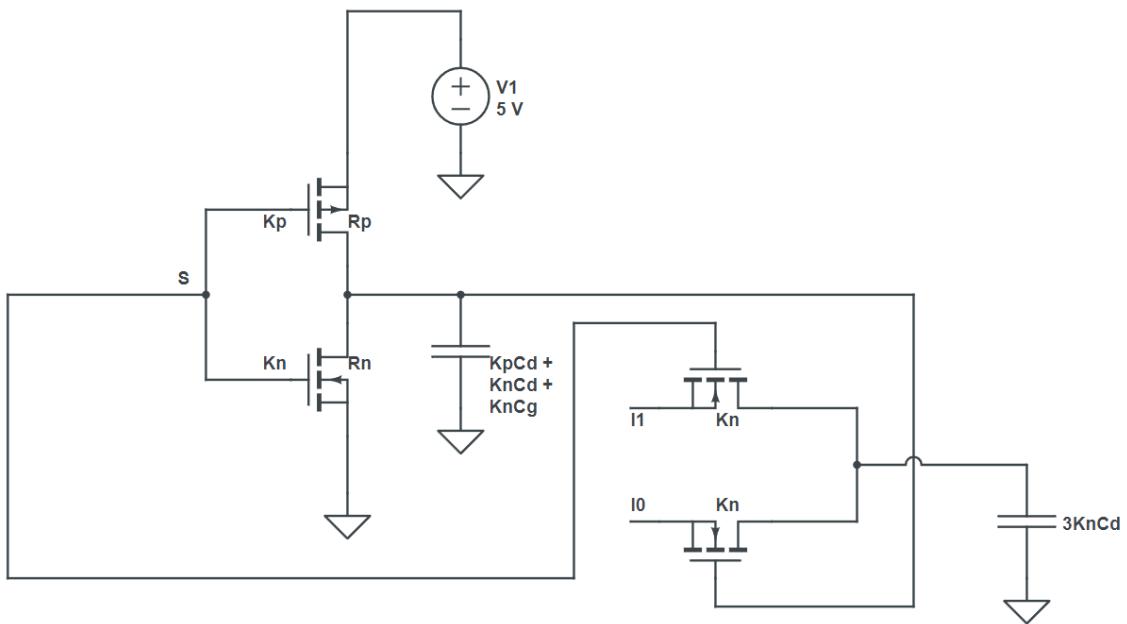


The worst case for the Elmore delay is when the PMOS in the inverter is ON, and '1' passes through 'I0'.

$$\tau_p = 0.69 \left(\frac{R_p}{k_p} (k_p C_d + k_n C_d + k_n C_g) + \frac{R_n}{k_n} (3k_n C_d) \right)$$

$$\tau_p = 0.69 \left(R_p C_d + R_p \frac{k_n}{k_p} C_d + R_p C_g + 3R_n C_d \right)$$

$$\tau_p = 0.69 \left(R_p \left(\left(C_d + \frac{k_n}{k_p} C_d \right) + C_g \right) + 3R_n C_d \right)$$

Stage 2 - 16:1 Mux (Device Under Test)

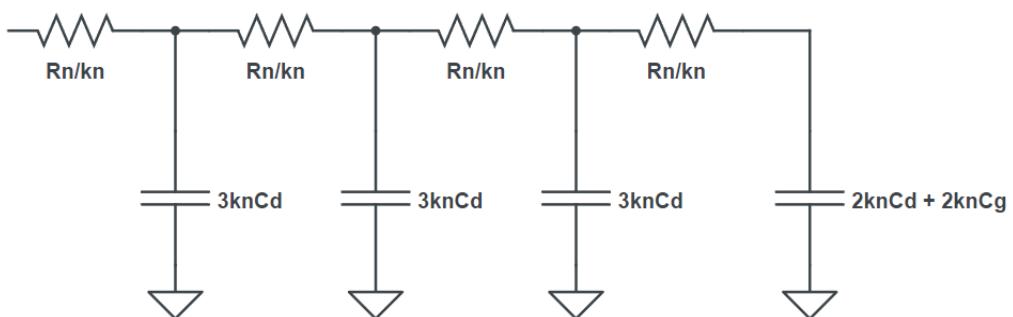

The RC Delay circuit for the 16:1 Mux is shown above. At any point in time only 1 of the multiplexers in each stage will be switched ON, and hence they will contribute to the delay.

$$\tau_p = 0.69 \left(\frac{R_n}{k_n} (3k_n C_d) + \frac{2R_n}{k_n} (3k_n C_d) + \frac{3R_n}{k_n} (3k_n C_d) + \frac{4R_n}{k_n} (2k_n C_d + k_n C_g + k_p C_g) \right)$$


$$\tau_p = 0.69 \left(26R_n C_d + 4R_n C_g + 4R_n \frac{k_p}{k_n} C_g \right)$$

The delay for the 4 inverters that are placed for driving the select lines of our 16:1 mux also needs to be added. The last stage consisting of 8 multiplexers becomes the worst case, since the select line needs to drive 8 multiplexers. Also, the path that goes via \bar{S} , will be the one that is considered since the inverter is also a part of it. Hence, that delay will need to be included in our calculations.

The resulting equation then comes out to be,

$$\tau_p = 0.69 \left(\left(26R_n C_d + 4R_n C_g + 4R_n \frac{k_p}{k_n} C_g \right) + 4 \left(\frac{R_n}{k_n} (9C_g + k_p C_g + k_p C_d + k_n C_d) \right) \right)$$

Stage 3 – Restoration with Buffer

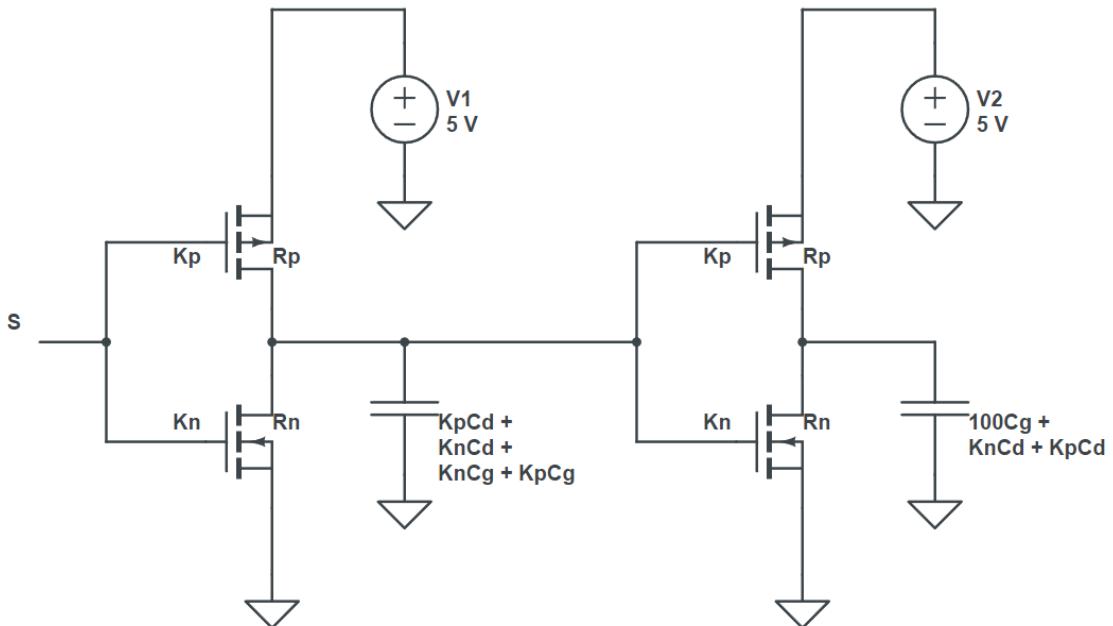

Finally, the delay for the restoration stage is calculated. Here we assume the output is '1' and therefore the 'NMOS' for the first inverter will be switched 'ON' and the 'PMOS' for the second inverter will be 'switched ON'.

$$\tau_p = 0.69 \left(\frac{R_n}{k_n} (k_n C_g + k_p C_g + k_n C_d + k_p C_d) + \frac{R_p}{k_p} (100C_g + k_n C_d + k_p C_d) \right)$$

Complete Delay

Putting together the delay for the 1st, 2nd and 3rd stage we obtain the complete delay equation,

$$\begin{aligned}\tau_p = & 0.69 \left(R_p \left(\left(C_d + \frac{k_n}{k_p} C_d \right) + C_g \right) + 3R_n C_d \right) \\ & + 0.69 \left(\left(26R_n C_d + 4R_n C_g + 4R_n \frac{k_p}{k_n} C_g \right) \right. \\ & \left. + 4 \left(\frac{R_n}{k_n} (9C_g + k_p C_g + k_p C_d + k_n C_d) \right) \right) \\ & + 0.69 \left(\frac{R_n}{k_n} (k_n C_g + k_p C_g + k_n C_d + k_p C_d) + \frac{R_p}{k_p} (100C_g + k_n C_d + k_p C_d) \right) \\ \tau_p = & 0.69 \left\{ R_n \left[C_d \left(34 + 5 \frac{k_p}{k_n} \right) + C_g \left(4 + \frac{36}{k_n} + 9 \frac{k_p}{k_n} \right) \right] + R_p \left[C_d \left(2 + 2 \frac{k_n}{k_p} \right) + C_g \left(\frac{100}{k_p} + 1 \right) \right] \right\}\end{aligned}$$

It can be seen from the equation above that if we assume $k_p = k_n = k$, the expression for τ_p reduces to,

$$\begin{aligned}\tau_p = & 0.69 \left\{ R_n \left[C_d (34 + 5(1)) + C_g \left(4 + \frac{36}{k} + 9(1) \right) \right] + R_p \left[C_d (2 + 2) + C_g \left(\frac{100}{k} + 1 \right) \right] \right\} \\ \tau_p = & 0.69 \left\{ R_n \left[39C_d + C_g \left(13 + \frac{36}{k} \right) \right] + R_p \left[4C_d + C_g \left(\frac{100}{k} + 1 \right) \right] \right\}\end{aligned}$$

This shows that k is inversely proportional to the delay and therefore as k increases the value for delay decreases.